

OM

Sujal N. Patel (~~XXXXXXXXXX~~)
ECE
• 9574 234 622

PM1(B)
ACE E. C. E

Dr. Chakrapani


Advanced Books

- ① Samuel C. Lee
- ② Rohavi
- ③ Bogert

Text Books

- ✓ ① Morris Mano.
- ② Tocci & Woolmer.
- ③ R.P. Jain

Digital Electronics

 

* Basic Topics


- ① Logic gates
- ② Number System
- ③ Complementary Number representation and Binary Number.
- ④ Binary codes.
- ⑤ Boolean Algebra.
- ⑥ k-maps.

★ Logic Gate:

→ AND, OR, NAND, NOR, EX-OR, EX-NOR gates.

→ NAND & NOR are Universal gates.

 ① Equivalence / coincidence gate
⇒ EX-OR gate



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$Y = A \odot B$$

$$\therefore Y = \bar{A} \cdot \bar{B} + A \cdot B$$

② Staircase Connection :-

⇒ EX-OR gate Logic

→





A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$$Y = A \oplus B$$

$$Y = \bar{A} \cdot B + \bar{B} \cdot A$$

③

  


$$\rightarrow A \oplus \bar{B} = A \odot B$$

④ Min no. of gates

	NAND	NOR
Ex-or	④	5
✓ EX-NOR	5	④

⑤

 


Control
'x' = 1


If $x = 1 \rightarrow Y = \bar{A}$ (Inverter)
 $x = 0 \rightarrow Y = A$ (Buffer).

NOTE: For X-NOR it reverse.

⑥

 
 
$$1 \oplus 1 \oplus 1 \oplus 0 \oplus 0 = 1$$



$$\downarrow$$

$$1 \odot 0 \odot 1 \odot 0 \odot 0 \odot 0 = 1$$

NOTE:

\rightarrow Ex-OR output = 1 if Input has odd no. of 1's
 \rightarrow Ex-NOR output = 1 if Input has Even no. of 0's.
 \rightarrow Ex-NOR = Ex-OR if no. of Input Variables are odd.
 E.g. = $A \oplus B \oplus C = A \odot B \odot C$


→ $E_{X-NOR} = \overline{E_{X-OR}}$

if no. of Input Variables
are even.

E.g. = $A \odot B \odot C \odot D = \overline{A \oplus B \oplus C \oplus D}$

⑦ Bubbled gates (Negative gates)


① Bubbled OR gate = NAND gate

 

② Bubbled AND gate = NOR gate





③ Bubbled EX-OR = EX-OR gate

 

⑧ Venn diagrams:


→ NOTE!

  


$$F = \bar{A} \cdot \bar{B} + A \cdot B$$

$$F = A \odot B \rightarrow \underline{\text{Ex-NOR gate}}$$


⑨

 


⑩

 


* ⑪

 

① Positive Logic

 


Negative Logic

 

e.g. ECL Logic
 
$$\Rightarrow \begin{aligned} '0' &= -1.8 \\ '1' &= -0.8 \end{aligned}$$



NOTE: In negative logic, more negative value treated as logic '1' state. e.g. $-1.8 \rightarrow \text{Logic '1'}$

Ex-1 If $A \cdot B = 0$; EX-OR gate behaves as logic '0'.

② _____ logic gates?

$$\rightarrow A \cdot B = 0$$

$$\Rightarrow A = 0, B = 1$$

$$A = 1, B = 0$$

$$A = 0, B = 0$$

$$A \cdot B = 1$$

$$A = 1, B = 1$$

$$\therefore A \oplus B = A\bar{B} + \bar{A}B = \overline{AB + \bar{A}\bar{B}} = \overline{0 + \bar{A}\bar{B}}$$

$$= A + B$$

$$= \text{OR gate}$$


Imp

NOTE:


In TTL Logic family open input is accepted by the logic gate as '1'.

(b) Find the value of $C = ?$

9

 

(c) Find output $F = ?$

 

$P=1$ $F=1$.

→ output at even gate is 1 and at odd gate is P'


→ After even no. gates → $o/p \Rightarrow 1$ } if $I/P = 0, 1$.

After 20 gates → $o/p = 1$.


if initial condition is reverse then 1 become 0 and it act as a buffer.

NOTE: Open Collector TTL will provide wired-AND operation.

for eg.

 

AND operation.

 


$$Y = A+B.C+D$$

Ex - 2 Determine the Logic represented by the following CKt.

(a) in +ve Logic.

(b) in -ve Logic.

 

A	B	Y
0	0	0V
+5	+5	+5V
+5	0	+5V
+5	+5	+5V

D_1, D_2, D_3 are ON.

D_2 ON, D_1 & D_3 are OFF

D_1 ON, D_2 & D_3 are OFF

D_1, D_2 ON, D_3 OFF.

$$Y = A + B = \text{OR gate.}$$

② Positive Logic.

+5V \rightarrow '1'

0V \rightarrow '0'

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

\Rightarrow OR gate.

⑥ Negative Logic

$+5 \rightarrow '0'$
 $0 \rightarrow '1'$


A	B	F
1	1	1
1	0	0
0	1	0
0	0	0

\Rightarrow AND gate.


NOTE: (i) $+ve$ logic OR gate = $-ve$ logic AND gate

$+ve$ logic	$-ve$ logic
AND \longrightarrow	OR
OR \longrightarrow	AND
NAND \longrightarrow	NOR
NOR \longrightarrow	NAND
EX-OR \longrightarrow	EX-NOR
EX-NOR \longrightarrow	EX-OR

⑥

 

⑦

 

NOTE:

- a) Diode pointing outwards \Rightarrow AND gate
b) Diodes pointing Inwards \Rightarrow OR gate

★ Number Systems: (Positional weighted Number system)

- 1) Decimal Base / Radix 10 (0, 1, 2, ..., 9)
2) Binary 2 (0, 1).
3) Hexadecimal 16 (0, 1, ..., 8, 9, A, B, C, D, E, F).
4) Octal 8 (0, 1, ..., 6, 7).

Ex-1 \rightarrow Digit '6' \Rightarrow Base ≥ 7 .

- $\cancel{b=6} \Rightarrow 0, 1, 2, 3, 4, 5, 6$
 $\checkmark b=7 \Rightarrow 0, 1, \dots, 6$
 $\checkmark b=8 \Rightarrow 0, 1, \dots, 6, 7$

$\checkmark \rightarrow$ Digit '9' \Rightarrow Base ≥ 10 .

\rightarrow Digit 'E' \Rightarrow Base ≥ 15 .

NOTE:

Diode pointing

$\rightarrow \leftarrow$

$\leftarrow \rightarrow$

+ve Logic

OR


AND

-ve Logic

AND

OR

① $1101101.10101_2 = X_{16}$

 

Ans: $(6D.A8)_{16}$

Ex-2 How many bits are required to represent 6728_{10} in binary.

Ans: $2^n > 6728_{10}$

$n = 13$ bits. $2^{12} = 4096$
 $2^{13} = 8192$

Ex-3 $6728_{10} \rightarrow X_2 =$
 \searrow
 X_{16}

16	6728	
16	420	8
16	26	4
	1	10 (A)

$(1A48)_{16} = (6728)_{10}$

Now, $1 \ A \ 4 \ 8$
 $\downarrow \ \downarrow \ \downarrow \ \downarrow$
 $0001 \ 1010 \ 0100 \ 1000$

$(6728)_{10} = (0001101001001000)_2$

Ex-3 How many bits are required to represent a 32 digit decimal no.?

Ans:

$$2^n > 10^{32}$$

$$\therefore n \ln 2 > 32 \ln 10$$

$$n > 32 \left(\frac{\ln 10}{\ln 2} \right)$$

$$n > 106.30 \Rightarrow \boxed{n=107}$$

Ex-4 Determine the base of the following relations.

② $24 + 17 = 40 \Rightarrow \text{max digit} = 7 \text{ hence base} \geq 8.$

Let, base = b

$$\therefore (2b^1 + 4b^0) + (1b^1 + 7b^0) = (4b^1 + 0)$$

$$\therefore 2b + 4 + b + 7 = 4b$$

$$\therefore \boxed{b = 11}$$

Note:

$$\begin{array}{l} 36_8 \xrightarrow{3 \times 8^1 + 6 \times 8^0} \\ AF_{16} \xrightarrow{10 \times 16^1 + 15 \times 16^0} \\ 24_b \xrightarrow{2 \times b^1 + 4 \times b^0} \end{array} \rightarrow X_{10}$$

(b) $\sqrt{41} = 5$

15

→ Let, Base = b.

$$\sqrt{4 \times b^1 + 1 \times b^0} = 5 \times b^0$$

$$\therefore 4b + 1 = 25$$

$$4b = 24$$

$$\therefore \boxed{b \neq 4}, \boxed{b = 6}$$

⚡
⚡
(c) Roots of $x^2 - 11x + 22 = 0$ are 3 and 6
b = ? Max digit = 6, Base ≥ 7 .

Ans:

$$x(x-3)(x-6) = 0$$

$$\therefore x^2 - 9x + 18$$

Let, roots are $x_1 = 3, x_2 = 6$.

$$\therefore x_1 + x_2 = -b/a$$

$$3_{base} + 6_{base} = -\frac{(-11)}{1} = 11_{base}$$

$$\therefore (3 \times base^0) + (6 \times base^0) = (base + 1)$$

$$\therefore 3 + 6 = base + 1$$

$$\boxed{base = 8}$$

(OR)

$$x_1 \cdot x_2 = c/a$$

$$\therefore 3_{b_1} \times 6_{b_1} = \frac{22}{1} = 22_{b_1}$$

$$\therefore 3 \times 6 = 2b_1 + 2$$

$$\therefore 18 = 2b_1 + 2$$

$$2b_1 = 16$$

$$\boxed{b_1 = 8}$$

Ex 5 What is the min decimal value of $11c_x = ?$

max digit c, so base ≥ 13 .

Ans:

$$(x^2 + x + 12x^0)_{10}$$

Base ≥ 13 .

$$= (x^2 + x + 12)_{10}$$

Min decimal occurs when base is minimum
i.e. $b = 13$.

$$\therefore = 13^2 + 13 + 12$$

$$= 194_{10}$$

Ex 6

$$\begin{array}{r} 1 \\ 1.24 \\ + 2.34 \\ \hline (10.1)_4 \end{array}$$

$$1. (2 \times 4^{-1}) = (1.5)_{10}$$

$$2. 3/4 = \frac{(2.75)_{10}}{4 \cdot 25}$$

↓

$$0.25 \times 4 = 1.0 \quad \uparrow$$

$$= 1 \quad 10. (2.75 + \frac{5}{16})$$

$$10.1.$$

Ex 7

$$\begin{array}{r} 3 \\ A80 \\ + 300 \\ \hline 200 \end{array}$$

$$B = 11$$

$$D = 13$$

$$24$$

$$A = 10$$

$$+ 3$$

$$+ 3$$

$$16$$

$$\begin{array}{r} 8 \overline{) 24} \\ 3 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 8 \overline{) 16} \\ 2 \\ \hline 0 \end{array}$$

Ex 8

A

b)

$$\begin{array}{r} \overset{1}{A} B_H \\ + 3 D_H \\ \hline (E8)_{16} \end{array}$$

$$\begin{array}{r} B = 11 \\ D = 13 \\ \hline (24)_{10} \end{array}$$

$$\begin{array}{r|l} 16 & 24 \\ \hline & 1 \end{array} \quad 8$$

$$(18)_{16}$$

17

$$\begin{array}{r} A = 10 \\ + 1 \\ + 3 \\ \hline 14 \end{array}$$

$$\begin{array}{r} \underline{E}_X - \underline{8} \\ b=1 \quad \overset{11}{1} D_H \\ \quad \quad 2 D_H \\ - A E_H \\ \hline - 7 F_H \end{array}$$

$$D = 13$$

$$E = 14$$

$$11_{16} \rightarrow 17_{10}$$

$$\therefore 17 - 10 = 7$$

$$\begin{array}{r} 1 D_H = 29_{10} \\ - E_H = -14_{10} \\ \hline F_H \leftarrow 15_{10} \end{array}$$

☆ Complementary Number Representation:

$$\rightarrow A - B = A + (-B)$$

$$A - B = A + (\text{Complement of } +B).$$

\rightarrow Base = 'r' system

$$\rightarrow (r-1)'s \text{ Complement} \Rightarrow r^n - r^{-m} - N$$

$$\rightarrow r's \text{ Complement} \Rightarrow r^n - N.$$

$\therefore N = \text{Given Number.}$

$n = \text{no. of digits in Integer part of } N.$

$m = \text{no. of digits in Fractional part of } N.$

E.g.: Find $r's$ Complement of $835.27_{10} = ?$

$$\rightarrow r = 10, N = 835.27, \leftarrow \text{method-1}$$

$$\therefore n = 3, m = 2.$$

$$= 10^3 - 10^{-2} - 835.27$$

$$= 1000 - 0.01 - 835.27$$

$$= 164.72_{10}$$

NOTE:

$$\begin{array}{r} 999.99 \\ - 835.27 \\ \hline (164.72)_{10} \end{array}$$

\leftarrow method:-2

Ex-2 10's Complement $(352)_{11} = ?$


Ans: $(352)_{11}$ $R=11$.

we have to find $(R-1)'s$ Comp.

$$\therefore \begin{array}{r} 10 \\ -3 \\ \hline 7 \end{array} \quad \begin{array}{r} 10 \\ -5 \\ \hline 5 \end{array} \quad \begin{array}{r} 10 \\ -2 \\ \hline 8 \end{array}$$

Ans: $= (758)_{11}$.

Ex-3 find 2's Comp. of $x = 101101000$

 

Ex-4 $0110_2 - 0001_2$
 $6_{10} - 1_{10}$

Ans: $0110_2 + (\text{Complement of } 0001)$.

→ By 1's complement

EAC

$$\begin{array}{r} 0110_2 = 6_{10} \\ + 1110 \leftarrow 1's \text{ Complement of } 0001_2 \\ \hline 0100 \\ \textcircled{1} \quad +1 \\ \hline 0101 = 5_{10} \end{array}$$

→ By 2's Complement.

$$\begin{array}{r} 0110_2 \\ + 1111 \leftarrow 2's \text{ Comp. of } 0001_2 \\ \hline 0101 = 5_{10} \end{array}$$

~~EAC~~ is discarded. $EAC = \text{End Around Carry.}$

D: 24/6/2013

NOTE:

→ EAC doesn't occur when the result is -ve. i.e. Large value is subtracted from a small value.



* 1's Comp. term

→ +0 = 0000

-0 = 1's Comp. of +0

= 1's Comp of 0000

→ -0 = 1111

2's Comp. term. ✓

→ +0 = 0000


→ -0 = 2's Comp. +0

= 2's Comp. 0000

→ -0 = 0000.

★ Binary Numbers:

→ 1) Unsigned numbers. ⇒

 

2) Signed numbers. ⇒ ✓

⇓



sign bit

0 → +ve

1 → -ve

⇒ @ signed magnitude form.

✓ (b) 1's complement form.

✓ (c) 2's complement form.

→ The Positive no. representation in all the above three forms is similar. 21

⇒ ① sign magnitude form.

$$+5_{10} = 0101$$

$$-5_{10} = 1101$$

② 1's Complement form.

$$+5_{10} = 0101$$

$$-5_{10} = 1's \text{ comp. of } +5$$

$$-5_{10} = 1010$$

③ 2's Complement form.

$$+5_{10} = 0101$$

$$-5_{10} = 2's \text{ comp. of } +5$$

$$-5_{10} = 1011$$

Ex-1 Represent the following no. in 2's complement form:

a) -17_{10} b) -83.375_{10}

Ans: a) $+17_{10} = 010001$ for +ve sign.

$-17_{10} = 2's \text{ comp. of } +17$

$= 101111$

-- 128 64 32 16 8 4 2 1.

0.5 0.25 0.125...

b) -83.375_{10}

→ $83.375 = 01000001.01010001.011$

$$\begin{aligned}
 \rightarrow -83.375_{10} &= 2^{\text{'s}} \text{ Comp. of } +83.375_{10} \\
 &= 2^{\text{'s}} \text{ Comp. } 01010011.011 \\
 &= (10101100.101)_2
 \end{aligned}$$

Ex-2
Determine the decimal values represented by the following signed no.s.

b) XXXX is ~~0101~~

1) Sign mag. no. 1101 is -5₁₀

$$\begin{array}{c}
 -5 = \begin{array}{c} 1101 \\ \downarrow \downarrow \\ -5 \end{array} = \begin{array}{c} 0101 \\ \downarrow \downarrow \\ +5 \end{array}
 \end{array}$$

2) (a) 2's Comp 01110 is +14

$$\begin{array}{c}
 \text{01110} \\
 \downarrow \downarrow \\
 +ve \quad +14
 \end{array}$$

b) 1's Comp no 01110 is +14

$$\begin{array}{c}
 01110 \\
 \downarrow \\
 +ve
 \end{array}$$

3) 2's Comp no. 11001 is ?

$$\begin{array}{c}
 11001 \\
 \downarrow \\
 -ve \quad \& \quad 2^{\text{'s}} \text{ Comp.}
 \end{array}$$

$$\begin{array}{c}
 \text{So,} \\
 \begin{array}{c} 11001 \\ \downarrow \\ -\text{sign } 2^{\text{'s}} \\ \rightarrow 00111 \\ = -7 \end{array}
 \end{array}$$

$$\begin{array}{c}
 \begin{array}{ccccc}
 4 & 3 & 2 & 1 & 0 \\
 -2^4 & 2^3 & 2^2 & 2^1 & 2^0 \\
 \text{1} & 1 & 0 & 0 & 1 \\
 \downarrow & \downarrow & & & \\
 = -16 + 8 + 1 \\
 = -7
 \end{array}
 \end{array}$$

4) 2's Comp. number 1000 is \Rightarrow -8?

23

$$\begin{aligned} \rightarrow & \quad 1000 \\ & = -8 + 0 + 0 + 0 \\ & = -8. \end{aligned}$$

$$\begin{aligned} & \quad \begin{array}{c} 1000 \\ \downarrow \text{2's comp} \end{array} \\ & \rightarrow 1000 \\ & = -8. \end{aligned}$$

5) 1's Comp. no 10010 is —?

Ans:

$$\begin{aligned} & \quad \begin{array}{c} 10010 \\ \downarrow \text{1's comp} \\ \rightarrow 01101 \end{array} \\ & = -13 \end{aligned}$$

$$\begin{aligned} & \quad \begin{array}{ccccc} 4 & 3 & 2 & 1 & 0 \\ -(2^4) & 2^3 & 2^2 & 2^1 & 2^0 \\ 1 & 0 & 0 & 1 & 0 \\ \downarrow \\ -16 & +0 & +0 & +2 & \\ = -13. \end{array} \end{aligned}$$

GATE

(1) What is the equivalent 2's Comp. representation of a 2's comp. no. 1101 is —?

$$\rightarrow \text{2's Comp. no.} \rightarrow \text{0011} \quad 1101. \Rightarrow -3$$

$$(A) \quad 101101 \rightarrow -19_{10}$$

$$\times (B) \quad 001101 \rightarrow +13_{10}$$

$$\checkmark (C) \quad 111101 \rightarrow -3_{10}$$


$$\times (D) \quad 011101 \rightarrow +23_{10}$$

$$\begin{aligned} & \quad \begin{array}{c} 111101 \\ \text{2's} \\ = 00001 \\ = -3. \end{array} \end{aligned}$$

* Sign bit Extension:

\rightarrow In 1's & 2's Complement form the Sign bit can be extended towards left any no. of times without changing its Value.


E.g. Consider 2's comp. no.

 

Ex: A 2's Comp. no. " $x_4 x_3 x_2 x_1$ " is copied into 8-bit register which of the following indicate the value of the register.

- (a) $11 x_4 x_3 x_2 x_1$.
- ✓ (b) $x_4 x_4 x_4 x_3 x_2 x_1$.
- (c) $00 x_4 x_3 x_2 x_1$.
- (d) None.

* Convert Byte to word (~~CWB~~ CBW).

 

2) Convert Word to Double word. \Rightarrow (CWD).

\downarrow \downarrow
16 bit 32 bit

Ex. 2
 \Rightarrow A register contain a 2's comp. no.

25

10100. it is divided by 2 find the value of the reg.

Ans:

10100

$$= -16 + 4 = -12$$

$$\therefore \frac{-12}{2} = -6$$


\therefore 2's comp = 6

$$-6 = 2's \text{ Comp. } +6$$


$$= 2's \text{ Comp. } 00110$$

$$= 11010$$


method-2:

 

Ex. 3

 

 Overflow (Range of 2's Comp. nos. using 5 bit is exceeded.)





Range of number represents using 'n' bits.

1's Comp.

form

$$+ (2^{n-1} - 1) \text{ to } - (2^{n-1} - 1)$$

Sign mag. form

e.g. $n=5 \rightarrow +15_{10} \text{ to } -15_{10}$

2's Comp

form

$$+ (2^{n-1} - 1) \text{ to } -2^{n-1}$$

e.g. $n=5 \Rightarrow +15_{10} \text{ to } -16_{10}$

Note:


Range of sign mag. form

= Range of 1's Comp. form.



Binary Codes:

7bit ASCII code in serial fashion.

 

xxx xxxx




zero \rightarrow '0' \Rightarrow $30_H = \boxed{011\ 0000_2}$

'A' \Rightarrow $41_H = \boxed{100\ 0001_2}$

'a' \Rightarrow $61_H = \boxed{110\ 0001_2}$

(1) Alphanumeric Codes.


(2) Numeric Codes.

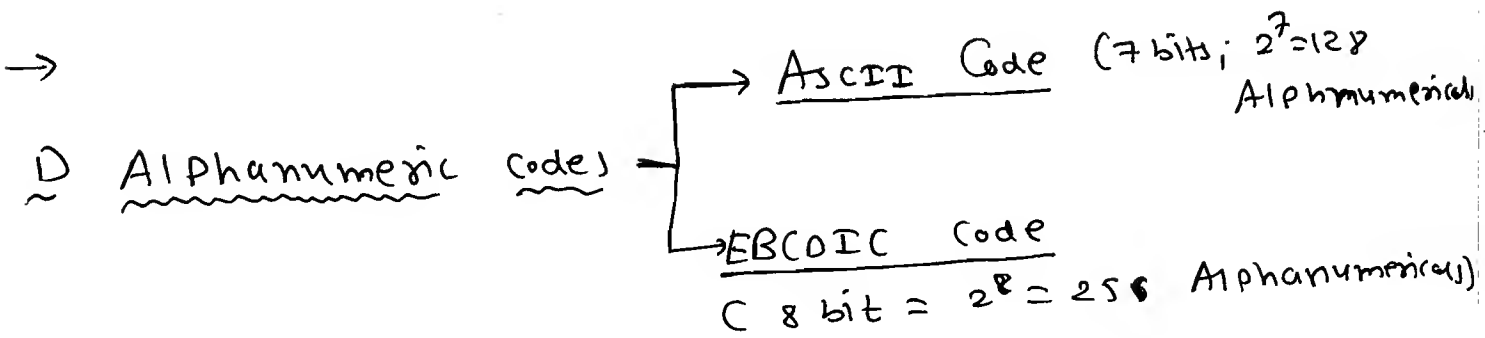

→ used in IBM Computers.

2) Numeric Codes:

→ BCD (Binary Coded Decimals) codes.

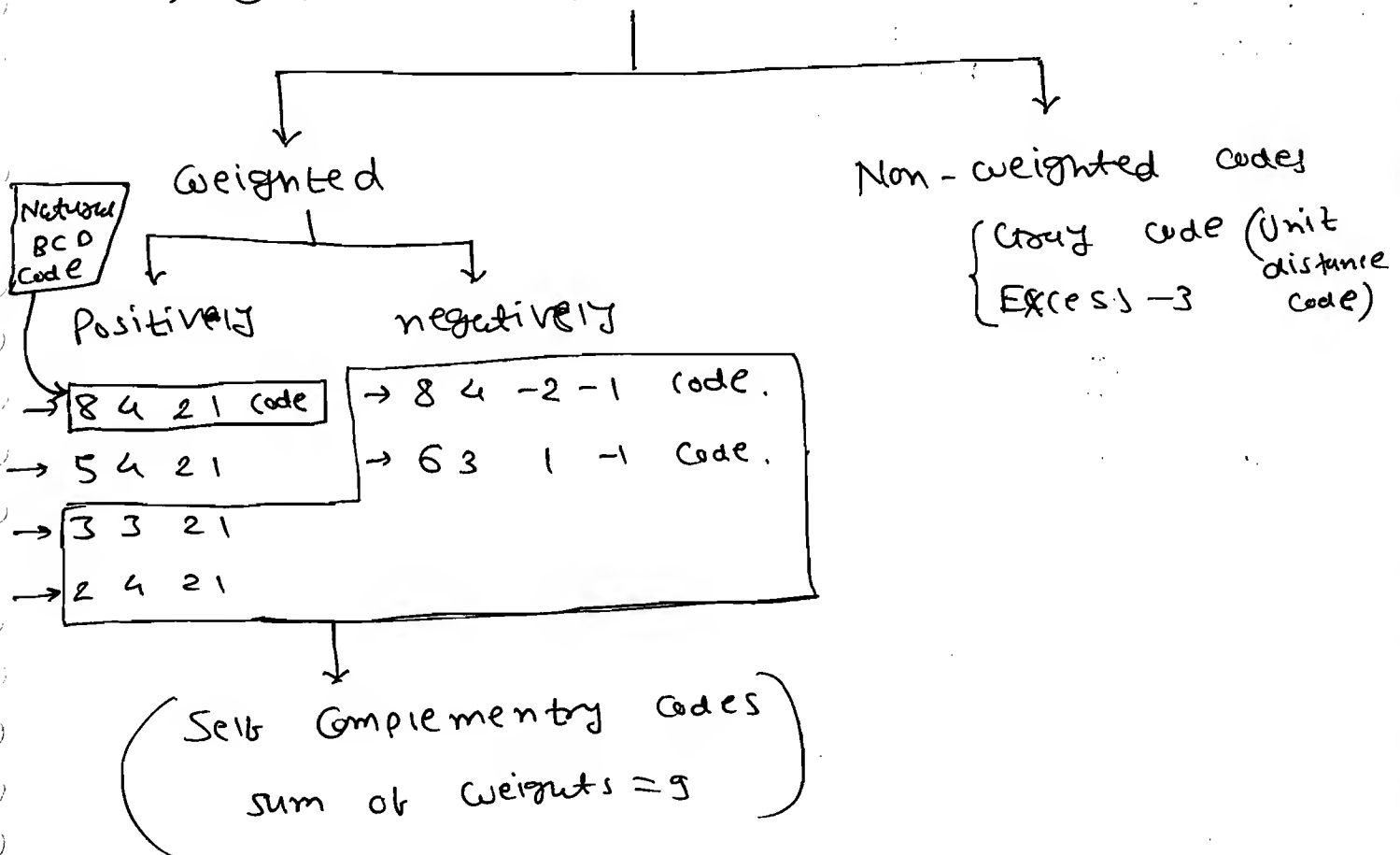

Decimal Digit	8 4 2 1	Excess-3
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0
Invalid BCD	1 0 1 0 1 0 1 1 1 1 0 0 1 1 0 1 1 1 1 0 1 1 1 1	

(1) Self Complementary.

8421	Ex-3
$3_{10} = 0011$ 9's Comp $6_{10} = \cancel{0000} = 0110$	$0110 \rightarrow 3_{10}$ $1001 \rightarrow 6_{10}$ 1's Comp.

(2) Sequential Codes:

8421	Ex-3
$3_{10} \rightarrow 0011$ $+ 1$ $4_{10} \rightarrow 0100$ $+ 1$ $5_{10} \rightarrow 0101$	$0110 \leftarrow 3_{10}$ $+ 1$ $0111 \leftarrow 4_{10}$ $+ 1$ $1000 \leftarrow 5_{10}$

→ The advantage of Ex-3 code is
it is both sequential and self complementary.

→ During BCD addition output is invalid

✓ (1) If the result is greater than 9

✓ (2) If carry occurs during BCD addition

E.g. $68_{10} \rightarrow$ $\begin{array}{c} 1111 \text{ (Carry = 1)} \\ 0110 \end{array} 1000$ Invalid

$$\begin{array}{r} + 58_{10} \\ \hline 126_{10} \end{array} \quad \begin{array}{r} + 0101 \ 1000 \\ \hline 1100 \ 0000 \\ + 0110 \ 0110 \\ \hline 10010 \ 0110 \end{array}$$

> 9
↓
Invalid

Ans → 126_{10}

(2) Find the no. of BCD correction = ?

@ 174_{10}
 $+ 826_{10}$

 1000

$$\begin{array}{r} 0001 \ 0111 \ 0100 \\ + 1000 \ 0010 \ 0110 \\ \hline 1001 \ 1001 \ 1010 \rightarrow > 9 \times \end{array}$$

$$\begin{array}{r} + 0110 \\ \hline 1001 \ 1010 \ 0000 \end{array}$$

$$\begin{array}{r} + 0110 \ 0000 \\ \hline 1010 \ 0000 \ 0000 \end{array}$$

$$\begin{array}{r} + 0110 \ 0000 \ 0000 \\ \hline 1000 \ 0000 \ 0000 \end{array}$$


1 0 0 0

= 1000_{10}

So, 3 correction

* Excess-3 Addition

→ Shuttl encoders

 

8421
7 → 0111
8 → 1000

More chance to
get error (or)
All 4 bit should
change


Gray code

0100 }
↓
1100 }

↓
Less chance to
get error ~~or~~ or
it is unit distance
code.

★ Code Conversion

① Binary to Gray.

 

$$\begin{aligned} G_4 &= B_4 \\ G_3 &= B_4 \oplus B_3 \\ G_2 &= B_3 \oplus B_2 \\ G_1 &= B_2 \oplus B_1 \end{aligned}$$

→ EX-OR → Modulo - 2 Addition


$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0$$

(2) Gray to Binary.

 

$$B_4 = G_4$$

$$B_3 = B_4 \oplus G_3$$

$$B_2 = B_3 \oplus G_2$$

$$B_1 = B_2 \oplus G_1$$

Ex-1 Represent $(743)_8$ in Gray code.

Ans:

$$(743)_8 \downarrow$$

$$\left(\frac{111}{7} \frac{100}{4} \frac{011}{3} \right)_2$$


Now B: 1 1 1 1 0 0 0 1 1

~~G: 1 1 1 1 0 0 0 1 1~~

G: ~~1 1 1 1 0 0 0 1 1~~ $(100010010)_2$

$\therefore (743)_8 = 100010010 \leftarrow \text{Gray code.}$

 Ex-2 Identify the following Code Converter.



$$Y_4 = X_4$$

$$Y_3 = X_4 \oplus X_3$$

$$Y_2 = X_4 \oplus X_3 \oplus X_2$$

$$Y_1 = X_4 \oplus X_3 \oplus X_2 \oplus X_1$$

$\& \text{ } G \rightarrow B$

Ex-3 $b_4 b_3 b_2 b_1$ is a 4-bit binary no. 33

What is the 6^n of the following eqⁿs.

(1) $b_{11} = b_1$


$b_{22} = b_1 \oplus b_2$

$b_{33} = (b_1 + b_2) \oplus b_3$

$b_{44} = (b_1 + b_2 + b_3) \oplus b_4$

b_1	b_2	b_3	b_4
0	1	0	1
0	1	1	0
0	1	1	0
1	0	1	0
0	1	1	0

So, Ans is 2's Complement.

 

* Hamming Code (Single Error Correcting Code):

→ $2^k \geq m + k + 1$

m = no. of message bits.

k = no. of parity bits.

E.g. $m=4 \Rightarrow$ No. of Parity bits $k=3$

Let, m_1, m_2, m_3, m_4

Let, P_1, P_2, P_3

001	010	011	100	101	110	111
$2^0 = 1$	$2^1 = 2$	3	$2^2 = 4$	5	6	7
P_1	P_2	m_1	P_3	m_2	m_3	m_4

✓ Choose ' P_1 ' such that 1, 3, 5, 7 = P_1, m_1, m_2, m_4 has odd parity

✓ Choose ' P_2 ' such that 2, 3, 6, 7 = P_2, m_1, m_3, m_4 " " "

✓ Choose ' P_3 ' such that 4, 5, 6, 7 = P_3, m_2, m_3, m_4 has odd parity.

★
Ex-1 (7,4) Hamming Code with odd parity
for the message 1001.

①
→ 7 = total no. of bits.
4 = no. of message bits.

∴

	1	2	3	4	5	6	7
P_1		P_2	1	P_3	0	0	1

Choose $P_1 = P_1, 1, 0, 1$ Should have ^{odd} parity ~~⇒ 1~~
1, 3, 5, 7 ⇒ Choose $P_1 = 1$

Choose P_2 2, 3, 6, 7 = P_2 1 0 1 " " " "
 $P_2 = 1$

Choose P_3 4, 5, 6, 7 = P_3 0 0 1 " " " "
 $P_3 = 0$

Corrected code: 1 1 1 0 0 0 1

② (7,4) code hamming code is received as

1 1 1 0 1 0 1

Ans: 4, 5, 6, 7 ⇒ 0 1 0 1 ⇒ even parity ⇒ $C_3 = 1$
(in error)

2, 3, 6, 7 ⇒ 1, 1, 0 1 ⇒ odd parity ⇒ $C_2 = 0$

1, 3, 5, 7 ⇒ 1, 1, 1, 1 ⇒ even parity ⇒ $C_1 = 1$
(in error)

i.e. error occurred at $C_3 C_2 C_1 = 1 0 1 = 5^{\text{th}}$ position.

Received Code = 1 1 1 0 1 0 1
Corrected code = 1 1 1 0 0 0 1 = 1001.
transmitted code

⇒ For Hamming Distance

a) For Correcting

't' errors:

$$\text{Hamming distance} \geq 2t+1.$$

b) For detecting

't' errors:

$$\text{Hamming distance} \geq t+1.$$

☆ Boolean Algebra:

⇒

'AND' Law

'OR' Law

Identity element ⇒ '1'

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

'0'

$$A + 0 = A$$

$$A + 1 = 1.$$

② Commutative Law:

③ Dual $\left\{ \begin{array}{l} A + B = B + A \\ A \cdot B = B \cdot A \end{array} \right.$

NAND : ↑

$$A \uparrow B = B \uparrow A$$

$$\therefore \overline{A \cdot B} = \overline{B \cdot A}$$

④ Dual $\rightarrow A \downarrow B = B \downarrow A$

⇒ Inhibition: (/)

$$\Rightarrow x|y = x \cdot \bar{y}$$

✓

$$\boxed{\begin{array}{l} A|B \neq B|A \\ \therefore A \cdot \bar{B} \neq B \cdot \bar{A} \end{array}}$$

→ 'Inhibition is not Commutative.'

⑥ Associative Law:

Proof

$$\begin{array}{l} (A+B)+C = A+(B+C) \\ (A \cdot B) \cdot C = A \cdot (B \cdot C) \end{array}$$

$$\overset{1}{(A \uparrow B)} \overset{0}{\uparrow} C \neq \overset{0}{A \uparrow} (\overset{1}{B \uparrow} \overset{0}{C})$$

$$\begin{array}{c} 0 \uparrow 0 \\ = 1 \end{array}$$

$$\begin{array}{c} 1 \uparrow 1 \\ = 0 \end{array}$$

→ The NAND and NOR operation are Commutative but not Associative.

⑦ Consensus Law:

$$\underline{A} \cdot \underline{B} + \underline{\bar{A}} \cdot \underline{C} + \underline{B \cdot C} = A \cdot B + \bar{A} \cdot C$$

$$\therefore A \cdot B + \bar{A} \cdot C + B \cdot C (A + \bar{A})$$

$$= \underline{A \cdot B} + \underline{\bar{A} \cdot C} + \underline{ABC} + \underline{\bar{A}BC}$$

$$= \underline{A \cdot B} + \underline{\bar{A} \cdot C} +$$

$$= ABC(1+C) + \bar{A}C(1+C)$$

$$= AB + \bar{A}C$$

$$\underline{x} \cdot \underline{y} + \underline{\bar{y}} \cdot \underline{z} + W V \underline{x} \underline{z} = \underline{x} \cdot \underline{y} + \underline{\bar{y}} \cdot \underline{z}$$

Dual $(\underline{A+B}) \cdot (\underline{\bar{A}+C}) \cdot (\underline{B+C}) = (\underline{A+B}) \cdot (\underline{\bar{A}+C})$

(4) Distribution Law:

→ $A \cdot (B+C) = AB + AC$
Dual $A + (B \cdot C) = (A+B) \cdot (A+C)$

i) $\underline{\bar{X}} + \underline{X} \underline{\bar{Y}} = (\underline{\bar{X}} + \underline{X}) (\underline{\bar{X}} + \underline{\bar{Y}})$

$$\therefore \underline{\bar{X}} + \underline{X} \underline{\bar{Y}} = \underline{\bar{X}} + \underline{\bar{Y}}$$

(ii) $\underline{AB} + \underline{\bar{A}B} \underline{C} = (\underline{AB} + \underline{\bar{A}B}) (\underline{AB} + \underline{C})$
 $= \underline{AB} + \underline{C}$

(5) Transposition Law:

→ $\underline{AB} + \underline{\bar{A}C} = (\underline{\bar{A}+B}) (\underline{A+C})$

$$= \underline{\bar{A}} \cdot \underline{A} + \underline{\bar{A}} \underline{C} + \underline{AB} + \underline{BC}$$

$$= \underline{AC} + \underline{AB} + \underline{BC}$$

$$= \underline{\bar{A}C} + \underline{AB} \quad (\because \text{Consensus Law})$$

$$= \text{L.H.S}$$

→ $\underline{x \cdot y} + \underline{\bar{y} \cdot z} = (\underline{x + \bar{y}}) (\underline{y + z})$

⑥ De Morgan's Law:

→ (a) NOR gate = Bubbled AND gate

$$\overline{A+B+C+\dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$$

→ (b) NAND gate = Bubbled OR gate

$$\overline{A \cdot B \cdot C \cdot D \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \bar{D} + \dots$$

⑦ Shannon's Law:

→ To find Complement of a fun 'F'.

- (i) Find the Dual of F i.e. 'F_D'.
- (ii) Complement all variables.

Ex-1 $F = AB + BC + CA$ then $\bar{F} = \bar{A} \cdot \bar{B} + \bar{B} \cdot \bar{C} + \bar{C} \cdot \bar{A}$
[J(F)]

Ans:

$$F = AB + BC + CA$$

$$\therefore \bar{F} = (\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{C} + \bar{A})$$

$$= (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C}) (\bar{C} + \bar{A})$$

$$= \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}$$

$$= \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C}$$

$$i) F_D = (A+B) \cdot (B+C) \cdot (C+A)$$

$$(ii) \quad \bar{F} = (\bar{A} + \bar{B}) (\bar{B} + \bar{C}) (\bar{C} + \bar{A})$$

$$= (\bar{B} + \bar{A}\bar{C}) \cdot (\bar{C} + \bar{A})$$

$$= \bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A}\bar{C}$$

$$\therefore \bar{F} = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A}$$

☆☆

Ex-2 Simplify the following boolean expression to four literals.

$$(1) \quad F = \underline{\bar{A}C} + \underline{\bar{C}D} + \underline{\bar{B}C} + \underline{AB} \rightarrow \underline{4 \text{ literals.}}$$

Note: Literals: variable (or) complement of variables.

$$\text{Eg: } F(A, B, C) \Rightarrow \underline{A, \bar{A}, B, \bar{B}, C, \bar{C}}$$

$$F = (\bar{A} + \bar{B})C + \bar{C}D + AB$$

$$F = \underline{\bar{A}\bar{B}} \cdot C + \bar{C}D + \underline{AB}$$

$$\therefore F = AB + \underline{C} + \underline{\bar{C}D}$$

$$\boxed{F = AB + C + D}$$

Ex-3 Determine the number of two input NAND gates required to implement the following:

$$\text{Ans: } (1) \quad F = (\bar{X} + \bar{Y})(W + Z)$$

$$F = \overline{\overline{PW} \cdot \overline{PZ}}$$

$$\therefore \bar{F} = \underline{\overline{(\bar{X} + \bar{Y})} \cdot \overline{(W + Z)}}$$

4 NAND gates req.

$$F = \bar{X} \cdot \bar{Y} (W + Z)$$

$$\therefore F = \frac{\bar{X} \cdot \bar{Y} W + \bar{X} \cdot \bar{Y} \cdot Z}{PW + PZ} \quad P = \underline{\bar{X} \cdot \bar{Y}}$$


$$(b) F = A + AB + ABC.$$

$$= A + AB(1+C).$$

$$= A + AB.$$

$$= A(1+B)$$

$$\therefore \boxed{F = A}$$

 

'0' NAND gates.

\Rightarrow 0 NAND gate is required.

~~★~~
~~★~~

(c) n -input AND gate = ?

NAND gates

$$\rightarrow 2 \text{ i/p AND } \Rightarrow F = \overline{\overline{A \cdot B}} = \textcircled{2}$$

$$3 \text{ i/p AND } \Rightarrow F = \overline{\overline{ABC}} = \textcircled{4}$$

$$4 \text{ i/p AND } \Rightarrow F = \overline{\overline{ABCD}} = \textcircled{6}$$

\therefore
 $n \text{ i/p AND } \Rightarrow \text{for } (2n-2) \text{ no. of } 2 \text{ i/p NAND gates req.}$

Ex-~~q~~ Implement EX-OR gate using minimum no. of (a) NAND gate (b) NOR gate.

Ans:

$$\rightarrow A \oplus B = \bar{A} \cdot B + A \cdot \bar{B}$$


$$= \bar{A} \cdot B + \underline{\underline{A \cdot \bar{B}}} + \boxed{\underline{\underline{A \cdot \bar{A}}} + \underline{\underline{B \cdot \bar{B}}}}$$

$$= B(\bar{A} + \bar{B}) + A(\bar{A} + \bar{B})$$

$$= \underline{\underline{A \cdot \bar{A}B}} + \underline{\underline{B \cdot \bar{A}B}}$$

$$\overline{F} = \overline{A \cdot \overline{AB} + B \cdot \overline{AB}}$$
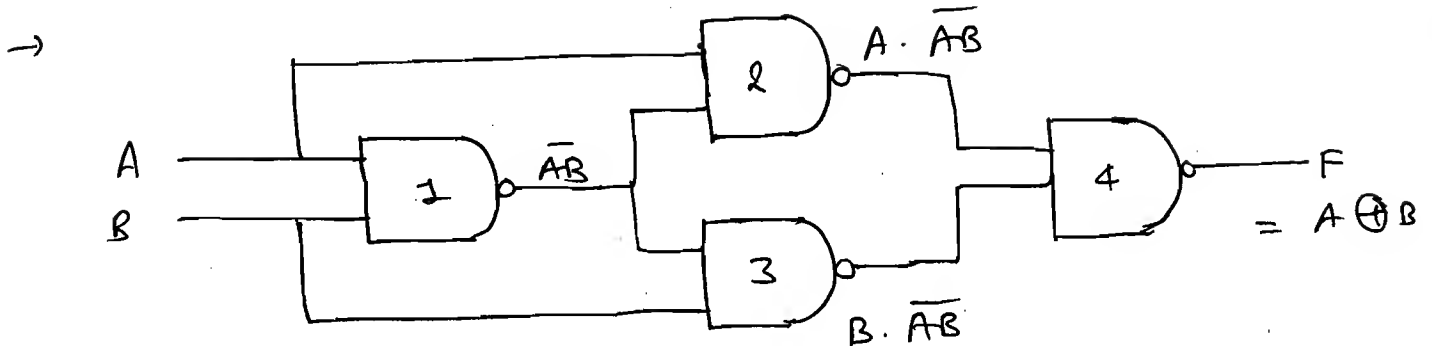
$$\therefore \overline{F} = \overline{A \cdot \overline{AB}} + \overline{B \cdot \overline{AB}}$$



(b) using Nor gate:

$$F = A \oplus B$$

$$F = \overline{A(\overline{A+B}) + B(\overline{A+B})}$$


$$\therefore \cancel{F} = \cancel{A(\overline{A+B})} + \cancel{B(\overline{A+B})}$$


$$\overline{F} = \boxed{(\overline{A+B})(A+B)} \quad \checkmark$$

$$= \overline{(\overline{A+B})(A+B)}$$

$$F = \overline{\overline{A+B}} + \overline{A+B}$$


∴ 5 Nor gate.

 

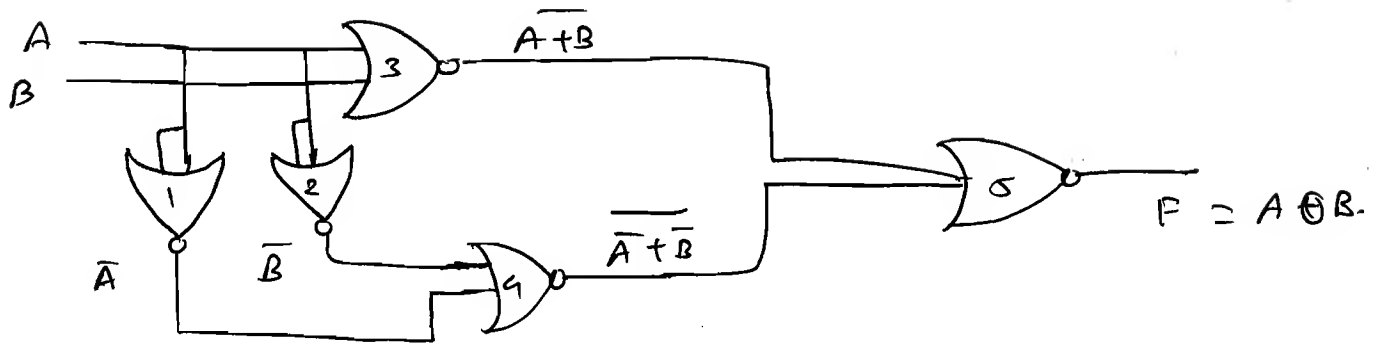


→ If Complement of I/P variables are given
 i.e. \bar{A} , \bar{B} are available then only 3 NOR
gates are required to implement $A \oplus B$.

* X-NOR using min. no. of NOR gates!

 

* X-NOR using min. no. NAND gates!

 

* Minterms, Maxterms & Properties.

→ Minterms → Standard Product term.

→ maxterms → Standard Sum term.

⇒ Minterms → 8

$$m_0 \quad \begin{array}{ccc} 0 & 0 & 0 \\ \bar{A} & \cdot & \bar{B} & \cdot & \bar{C} \end{array}$$

$$m_1 \quad \begin{array}{ccc} 0 & 0 & 1 \\ \bar{A} & \cdot & \bar{B} & \cdot & C \end{array}$$

$$m_2 \quad \begin{array}{ccc} 0 & 1 & 0 \\ \bar{A} & \cdot & B & \cdot & \bar{C} \end{array}$$

$$m_3 \quad \bar{A} \cdot B \cdot C$$

$$m_4 \quad A \cdot \bar{B} \cdot \bar{C}$$

$$m_5 \quad A \cdot \bar{B} \cdot C$$

$$m_6 \quad \begin{array}{ccc} 1 & 1 & 0 \\ A & \cdot & B & \cdot & \bar{C} \end{array}$$

$$m_7 \quad \begin{array}{ccc} 1 & 1 & 1 \\ A & \cdot & B & \cdot & C \end{array}$$

$$\text{Var} = 1$$

$$\overline{\text{Var}} = 0$$

Maxterms → 8

$$M_7 \quad \begin{array}{ccc} \phi & \phi & \phi \\ \bar{A} & + & \bar{B} & + & \bar{C} \end{array}$$

$$M_6 \quad \begin{array}{ccc} 1 & 1 & 0 \\ \bar{A} & + & \bar{B} & + & C \end{array}$$

$$M_5 \quad \begin{array}{ccc} 1 & 0 & 1 \\ \bar{A} & + & B & + & \bar{C} \end{array}$$

$$M_4 \quad \begin{array}{ccc} 1 & 0 & 0 \\ \bar{A} & + & B & + & C \end{array}$$

$$M_3 \quad \begin{array}{ccc} 0 & 1 & 1 \\ A & + & \bar{B} & + & \bar{C} \end{array}$$

$$M_2 \quad A + \bar{B} + C$$

$$M_1 \quad A + B + \bar{C}$$

$$M_0 \quad \begin{array}{ccc} 0 & 0 & 0 \\ A & + & B & + & C \end{array}$$

$$\text{Var} = 0$$

$$\overline{\text{Var}} = 1$$

Ex-1: $F(A, B, C, D, E)$ and find $m_{23} = ?$, $M_{19} = ?$

Ans:

$$m_{23} = \begin{array}{ccccc} & 1 & 0 & 1 & 1 & 1 \\ & \bar{A} & \cdot & \bar{B} & \cdot & C & D & E \end{array}$$

$$M_{19} = \begin{array}{ccccc} 1 & 0 & 0 & 1 & 1 \\ \bar{A} & + & B & + & \bar{C} & + & \bar{D} & + & \bar{E} \end{array}$$

* Properties:

① n-var Function \Rightarrow 2^n min terms
 2^n max terms.

② $M_j = \overline{m_j}$ and vice versa.

③ $m_i^D = M_{(2^n - 1 - i)}$ $D = \text{dual}$

e.g. $m_3 = \overline{A} B C$

$m_3^D = \overline{\overline{A} B C} = A + \overline{B} + \overline{C}$

✓

$\therefore = M_4$

$m_3^D = M_{2^3 - 1 - 3}$

④ (a) Sum of all min terms = 1

i.e. $\sum_{i=0}^{2^n-1} m_i = 1$

⑥ Product of all max terms = 0 i.e.

$\prod_{j=0}^{2^n-1} M_j = 0$

BEL ★★

Ex-1

How many min terms are present at the o/p of ^{6 i/p} Ex-OR gate: $2^{6-1} = 32$ no. of min terms.

Ans:

$A \oplus B = A \cdot \overline{B} + \overline{A} \cdot B$

$A \oplus B \oplus \overline{A} \oplus \overline{B} = A \cdot \overline{B}$

$A \oplus B = m_1 + m_2$ [2 out of 4 min terms]

$\therefore A \oplus B \oplus C = m_1 + m_2 + m_4 + m_3$ [4 out of 8 min terms]

$\therefore A \oplus B \oplus C$ output contains $= \frac{2^n}{2}$
 $= 2^{(n-1)}$ no. of output min terms

NOTE: Same for X-NOR.

Ex-2 How many boolean fⁿs can be formed using n-boolean variables?

Ans: 'n' Boolean variable \rightarrow Boolean functions $= 2^{2^n}$.
 \downarrow
 $x = 2^n$ minterms $\nearrow 2^x = 2^{2^n}$

$F(A, B)$

	AB	F ₀	F ₁	F ₂	F ₃	...	F ₁₅
m ₀ \leftarrow	00	0	0	0	0		1
m ₁ \leftarrow	01	0	0	0	0		1
m ₂ \leftarrow	10	0	0	1	1		1
m ₃ \leftarrow	11	0	1	0			1

\downarrow (Null)
 \downarrow AND
 \downarrow Inhibition (A/B)
 \downarrow Transfer
 \downarrow Identity.

* Forms of Boolean Functions:

- 1) a) Sum of Products (SOP) form. \rightarrow DNF
 b) Product of Sum (POS) form. \rightarrow CNF
- 2) a) Canonical (or) Standard SOP form. (Sum of minterms) \rightarrow DCF
 b) Canonical (or) Standard POS form. (Product of max terms) \rightarrow CCF

\checkmark DNF = Disjunctive Normal form

\checkmark CNF = Conjunctive normal form.

\checkmark DCF = Disjunctive canonical form

\checkmark CCF = Conjunctive Canonical form.

Ex-1 $F(A, B, C, D) = \bar{A} + \bar{A}C\bar{D} + \bar{B}C$ to Canonical SOP form.
(sum of minterms) form

Ans: $F(A, B, C, D) = \bar{A}B + \bar{A}\bar{B} + \bar{A}BC\bar{D} + \bar{A}\bar{B}C\bar{D} +$

$$F(A, B, C, D) = \bar{A} + \bar{A}C\bar{D} + \bar{B}C$$

	\bar{A}	$\bar{A}C\bar{D}$	$\bar{B}C$
	\downarrow	\downarrow	\downarrow
	\bar{A}	$\bar{A}C\bar{D}$	$\bar{A}B\bar{C}\bar{D}$
$m_0 \leftarrow$	0 0 0 0	0 0 1 0	0 0 1 1
\vdots	0 0 0 1	0 1 1 0	1 0 1 0 \rightarrow m_{10}
\vdots	0 0 1 0		0 1 0 1 \rightarrow m_{11}
\vdots	0 0 1 1		
\vdots	0 1 0 0		
\vdots	0 1 0 1		
\vdots	0 1 1 0		
m_7	0 1 1 1		


$\therefore F(A, B, C, D) = \sum m(0, 1, \dots, 7, 10, 11) \leftarrow$ Can SOP form.

$\therefore F(A, B, C, D) = \prod M(8, 9, 12, 13, 14, 15) \leftarrow$ Can POS form.

Ex-2 Convert $F(A, B, C) = A \cdot B + \bar{A} \cdot C$ into Canonical POS form (product of maxterms)

Ans: $F(A, B, C) = \bar{A} \cdot B + \bar{A} \cdot C$

$\bar{A} \cdot B$	$\bar{A} \cdot C$
\downarrow	\downarrow
m_0 0 0 0	M_4 1 0 0
m_1 0 0 1	M_5 1 0 1

 

$$F = A \cdot B + \bar{A} \cdot C$$

$$F = (A+B) \cdot (\bar{A}+C)$$

$$F = (\bar{A}+C) \cdot (\bar{A}+B)$$

$$F = \sum m(0, 2, 4, 5)$$

	A	B	C
m_0	0	0	0
m_2	0	1	0


	A	B	C
m_4	1	0	0
m_5	1	0	1

* Two Level Logic:


→ (a) SOP form:

$$F = AB + CD$$

AND-OR Logic

 



\equiv NAND-NAND Logic

 

(2) POS form:


$$F = (A+B) \cdot (C+D)$$

OR-AND Logic : \equiv NOR-NOR Logic

  

* Hybrid Logic.

$$F = AB + AC = A \cdot (B + C)$$

 

→ The advantages of two level logic is the propagation for all the input variables is same.


☆ Types of Two Level Logic:

- Ex. (1) Degenerative
(2) Non-Degenerative.

① Degenerative.

⇒ There are only one logical operation in o/p, then it is called Degenerative type.

e.g. NAND-NOR Logic

 

→ The advantages of Degenerative form is the number of the gate is increase.

★ Karnaugh Maps (Veitch Diagram). 49

* 3-Variable K-Map:

$F(A, B, C)$

		BC			
		00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6

Octet (group of 8 adj minterms).

Quad (group of 4 adj. minterms).

Pair (group of 2 adj minterms).

Q: How many possible ways to get one of minterm?

Ans: **6.**

* 4-Variable K-Map

		CD			
		00	01	11	10
AB	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

Possible Quads $\Rightarrow 24$

Possible Octets $\Rightarrow 8$

Possible Pairs $\Rightarrow 32$

(0, 2, 8, 10) \Rightarrow Quad

Columns

Rows

✓ 1, 2

1, 2

✓ 2, 3

2, 3

✓ 3, 4

3, 4

✓ 4, 1

4, 1

Ex-1 Simplify the following expression using mapping.

(a) $F(A, B, C) = \sum m(1, 4, 5, 6)$

→

	BC	00	01	11	10
A	0		1		
	1	1	1		1

$\therefore F = A\bar{C} + \bar{B}C$

(b) $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 8, 9, 10, 12, 14, 15)$

	CD	00	01	11	10
AB	00	1	1	1	
	01	1	1	0	1
	11	1			
	10	1	1		1

	CD	00	01	11	10
AB	00	1	1		1
	01	1	1		
	11	1		1	1
	10	1	1		1

(090)

	CD	00	01	11	10
AB	00	1	1		1
	01	1	1		
	11	1		1	1
	10	1	1		1

NOTE

The simplified expression obtained using 51
K-map is minimal but not unique.

Ex-1 a) $F(A, B, C) = \sum m(1, 2, 4, 7)$.

b) $F(A, B, C) = \sum m(0, 3, 5, 6)$.

Ans: 5

Q

	B \bar{C}	00	01	11	10
A	0		1		1
	1	1		1	0

A B C

m₁ 0 0 1

m₂ 0 1 0

m₄ 1 0 0

m₇ 1 1 1

$F = A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + ABC$

$F = \bar{B}(A\bar{C} + \bar{A}C) + A(\bar{B}C + BC)$

$\therefore F = A \oplus B \oplus C$

→ All minterms have odd no. of 1's.

→ All minterms have even no. of 0's.

b)

	B \bar{C}	00	01	11	10
A	0	1		1	
	1		1		1

$F = \sum m(1, 2, 4, 7)$

$\bar{F} = \sum m(0, 3, 5, 6)$

$\bar{F} = \bar{F} \cdot 1$

$\therefore F = A \odot B \oplus C$

$F_1 = \bar{F}$

Let $z = A \oplus B$
 $= A \odot B$

$F_1 = \overline{A \oplus B \oplus C} = \overline{A \odot B \oplus C}$

$\therefore F_1 = \overline{z \oplus C}$



$F_1 = A \odot B \oplus C$ (or)

$F_1 = A \oplus B \odot C$


→ Minterms doesn't have odd no. zeros and even no. of 1's.

Ex-2 Represent $F = A \oplus B \oplus C \oplus D$ in Sum of minterms (Canonical Sol form).

Ans: $F = A \oplus B \oplus C \oplus D$.

  


Ans: 8

 

$$F = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$

Hint: All above minterms have odd no. of ones.

Ex-3 Simplify the following terms: map:

 

$$F = \sum m(0, 3, 5, 8, 9, 10, 12, 15)$$

* All minterms contain even no. zeros


So, X-NOR gate.

$$F = A \odot B \odot C \odot D$$

Ex-4 In n-variable k-map a group of 2^m is form. How many literals the resulting minterms.

Ans:


→ 3-var k-map →

 

$$F = 1$$

So, 0 literals

→ 4-var k-map →

 

$$F = D$$

So, 1 literal.

→ n-var k-map → there are $n-3$ literals.
require for 8 minterms.

for pair → $n-1$ literals.


→ for Quad → $n-2$ literals.

for ~~min~~ octet → $n-3$ literals.

Ex-5 Determine the simplified pos expression of F where, $F = \sum m(0, 2, 3, 4, 8, 10, 11, 14)$.

Ans: for pos.
 
$$\therefore F = \prod M(1, 5, 6, 7, 9, 12, 13, 15).$$



for max term

$$0 \rightarrow \frac{\text{var}}{\text{var}}$$

$$F = (\bar{B} + \bar{D}) \cdot (C + \bar{D}) \cdot (\bar{A} + \bar{B} + \bar{C}) (A + \bar{B} + \bar{C}).$$

* Implicant:

→ (i) Prime Implicant &

(ii) Essential implicant

→ Implicant:

→ it is the set of all adjacent min terms.

E.g. octets, pairs.


* Prime Implicant:

→ It is an implicant which is not a subset of another implicant.

e.g.
(a)




(b)

 

All 4 are
prime implicants.

(c) CD
AB

 


All are prime implicants.

* Essential Prime Implicants:

55

→ It is a prime implicant which contains at least 1 minterms which is not covered by another prime implicant.

e.g.

 

 ← is non-essential prime implicant and remaining are essential prime implicant.

* Non-Essential Prime Implicants:

① Redundant P.I (RPI).

→ It is a non-essential prime implicant whose minterms are covered by all essential P.I.


② Selective prime implicant:

→ It is a non-essential prime implicant whose minterms are covered by at least one non-essential P.I.

* Minimal Expression = EPI's + (optional) SPI

Ex-1 Determine the essential P.I. and minimal expression for the following f^n .

 Ans: ① $F(A, B, C) = \sum m(0, 1, 2, 5, 6, 7)$.



EP I's \rightarrow Null

RP I's \rightarrow Null

SP I's \rightarrow ①, ②, ③, ④

⑤, ⑥, ⑦


(none)

Minimal expression = ① + ② + ③

(or)

= ④ + ⑤ + ⑥

 ⑥ $F(A, B, C, D) = \sum m(0, 1, 4, 5, 6, 8, 9, 10, 12, 14, 15)$



except
EP I's = ⑤, all


$\therefore F = ① + ② + ③ + ④ + ⑥ + ⑦$

$F = \bar{A}\bar{C} + B\bar{D} + A\bar{D} + \bar{C}\bar{B} + ABC$

★ Don't Care Condition:

→ In a digital system for a non-occurring i/p, the o/p can be considered as either 0 (or) 1 during its simplification and it is called the don't Care Condition.

$$F_{CA(B)} = \sum m(0, 2) + d(3).$$

 


AB	F
00	1
01	0
10	1
11	1/0

← don't care condition.

Ex-1 Design BCD to 9's Comp. of BCD Code converter.

Ans:

 

0000
⋮
1001

Don't care { 1011 → x
⋮
1111 → x

	BCD				g's Comp. of BCD			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0
2	0	0	1	0	0	1	1	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	0	0
6	0	1	1	0	0	1	0	0
7	0	1	1	1	0	0	1	1
8	1	0	0	0	0	0	0	1
9	1	0	0	1	0	0	0	0

(i) for W:

AB	CD			
	00	01	11	10
00	1	1		
01				
11				
10				

$$W = \bar{A} \bar{B} \bar{C}$$

(ii) for X:

$$X = \sum m(2, 3, 4, 5) + d(m(11, \dots, 15))$$

AB	CD			
	00	01	11	10
00			1	1
01	1	1		
11	x	x	x	x
10			x	x

$$X = B \bar{C}$$

$$(iii) Y = C$$

direct form T.T

$$(iv) Z = \bar{D}$$

direct form T.T

* NOTE:

→ The purpose of minimization is to reduce the number of logic gates and no. of inputs.

$$\text{Ex-1 (i) } F_1(A, B, C) = \sum m(0, 2, 3, 5, 7) + d(1, 6, 7).$$

$$(ii) F_2(A, B, C) = \sum m(0, 1, 2, 3, 6) + d(4, 5, 7).$$

$$\text{Find } F_3 = F_1 + F_2$$

$$F_4 = F_1 \cdot F_2$$

$$\text{Ans: (i) } \sum m(0, 2, 3, 5) + d(1, 6, 7)$$

	BC	00	01	11	10
A					
0		1	X	1	1
1			1	X	X

$$F_1 = \bar{A} + C + B$$

$$(ii) \sum m(0, 1, 2, 3, 6) + d(4, 5, 7).$$

	BC	00	01	11	10
A					
0		1	1	1	1
1		X	X	X	1

$$F_2 = 1$$

$$F_3 = F_1 + F_2 = 1 + (\bar{A} + C) = 1$$

$$F_4 = F_1 \cdot F_2 = F_1 = \bar{A} + C$$

(0/0)

$1 + d = 1$	$0 \cdot d = 0$
$0 + d = d$	$1 \cdot d = d$
$d + d = d$	$d \cdot d = d$

$$F_3 = F_1 + F_2 = \sum m(0, 1, 2, 3, 5, 6) + d(4, 7)$$

$$F_4 = F_1 \cdot F_2 = \sum m(\overset{0}{\cancel{4}}, 2, 3) + d(1, 6, 7, 5)$$




Ex-2 $F_1(A, B, C) = \sum m(0, 3, 5, 6) + d(2, 4, 7)$

$$F_2(A, B, C) = \sum m(1, 2, 3, 6) + d(0, 5, 7)$$


Ans: $F_3 = F_1 + F_2 = \sum m(0, 1, 2, 3, 5, 6) + d(2, 4, 7)$

$$F_4 = F_1 \cdot F_2 = \sum m(3, 6) + d(0, 2, 5, 7)$$

   Ex-3 Determine the waveform at the o/p of the following logic ckt.



Ex-2

 


$\rightarrow A \Rightarrow$

$B \Rightarrow$

$F \Rightarrow$

Actual op
 \downarrow
 $F \Rightarrow$

 


★

Digital Circuits

Combinational Ckt

Sequential Ckt

 

→ Outputs = $F(\text{Present I/P})$


E.g. = Code Converter,

Adder & Subtractor,

Decoder, MUX,

Mag. Comparators, PLA,

✓ Rom

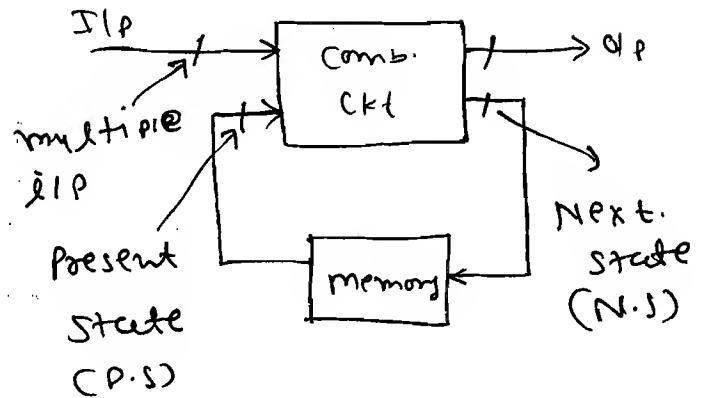

$O/P = F(\text{present state, present inputs})$

Next state = $F(\text{present state, present I/P.})$

→ Moores Seq Ckt.

$O/P = F(\text{present state only})$


$N.S. = F(\text{present Inputs, present state}).$

E.g. Shift register,
Counters, calculators,
MP, PC.

* Arithmetic Combinational Ckt.

53

(1) Half Adder:

 


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B}$$

$$S = A \oplus B$$


$$C = A \cdot B$$

⇒ Half Adder using NAND Gates.

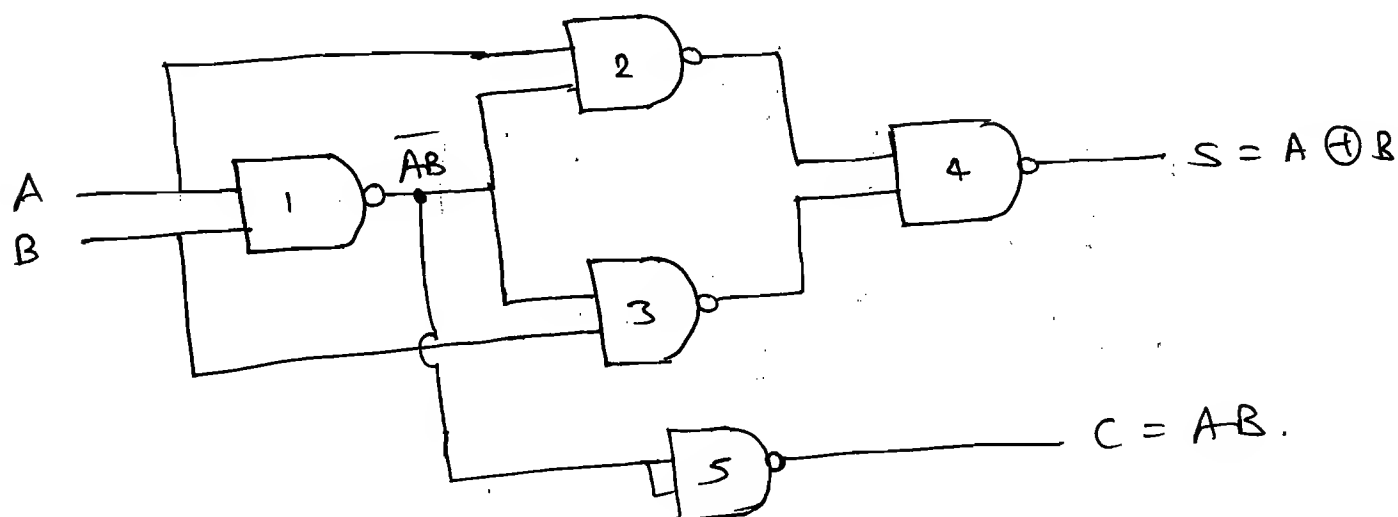


So, ⑤ NAND gate required.

⇒ Half Adder using NOR gate

 

So, ⑤ NOR gate required

(2) Half Subtractor:

 


A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = A \oplus B$$

$$B = \bar{A} \cdot B$$


$$\begin{array}{r} 10 \\ B - 1 \\ \hline 1 \rightarrow D \end{array}$$

⇒ Half Subtractor using NAND gate only:

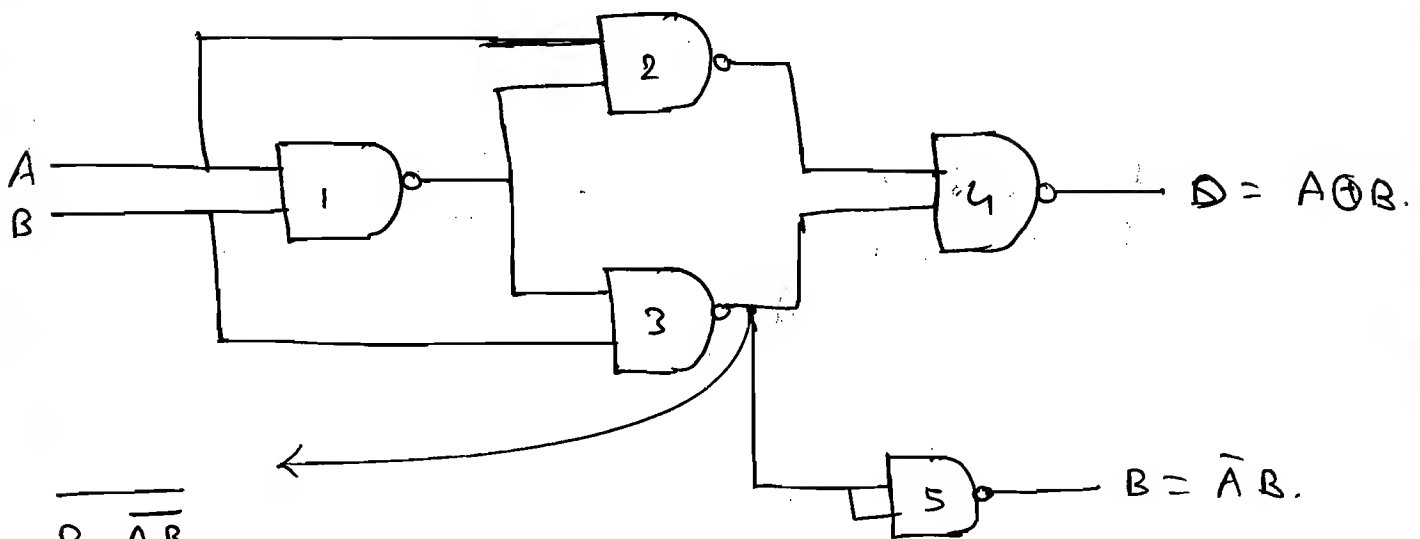


$$\begin{aligned} & \overline{B \cdot \bar{A} B} \\ &= \bar{B} + AB \\ &= A + \bar{B} = \overline{\bar{A} \cdot B} \end{aligned}$$

 
⇒ Half Subtractor using NOR gate only. 65



(3) Full Adder: (1 bit adder).

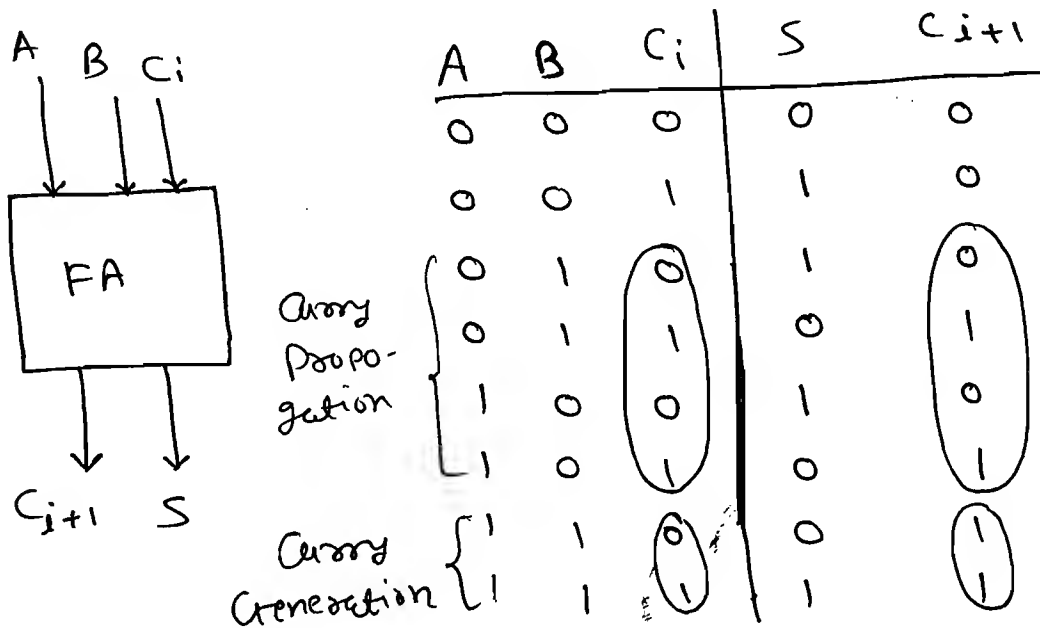

$$S(A, B, C_i) = \sum m(1, 2, 4, 7)$$

 

$$S = A \oplus B \oplus C_i \quad (\text{or}) \quad A \odot B \odot C_i$$

$$C_{i+1} = \sum m(3, 5, 6, 7)$$

$$= \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$$

$$= C_i (\bar{A}B + A\bar{B}) + AB$$

$$\therefore C_{i+1} = C_i (A \oplus B) + AB$$


	BC_i			
	00	01	11	10
A				
0			1	
1		1	1	1

$$C_{i+1} = AB + BC_i + AC_i$$

NOTE: Full adder

- (i) Require 9 NAND gate
- (ii) Require 12 NOR gate.

(4) Full Subtractor:

 

A	B	b_i	D	b_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\rightarrow D(A, B, b_i) = \sum m(1, 2, 4, 7).$$

	Bb_i			
	00	01	11	10
A				
0	0	1	1	1
1	1	0	0	1

$$D = A \oplus B \oplus b_i \text{ (or) } A \odot B \odot b_i.$$

$$\rightarrow b_{i+1}(A, B, b_i) = \sum m(1, 2, 3, 7).$$

$$b_{i+1} = m_1 + m_2 + m_3 + m_7$$

$$= \bar{A}\bar{B}b_i + \bar{A}B\bar{b}_i + \bar{A}Bb_i + ABb_i$$

$$= b_i(\bar{A}\bar{B} + AB) + \bar{A}B.$$

$$b_{i+1} = b_i(A \odot B) + \bar{A}B.$$

	Bb_i			
	00	01	11	10
A				
0	0	1	1	1
1	0	1	1	0

$$\therefore b_{i+1} = \bar{A}B + Bb_i + \bar{A}b_i$$


NOTE: Full subtractor

(i) Required 9 NAND gate


(ii) Required 12 NOR gate.

Ex-1 Implement Full Adder using HAs and Logic gate:

Ans:

 

\equiv

 

$$C_{i+1} = AB + C_i(A \oplus B)$$

1 Full adder = 2 Half adder + 1 OR gate

Ex-2 How many HA required to implement the following fⁿs.

$$F_1 = \bar{A}C + AB\bar{C} + \bar{B}C.$$

$$F_2 = A \oplus B \oplus C.$$

$$F_3 = \bar{A}BC + A\bar{B}C.$$

Ans: (i) $F_1 = \bar{A}C + AB\bar{C} + \bar{B}C.$

$$= \overline{AB} \cdot C + AB\bar{C}$$

$$= (\bar{A} \cdot \bar{B}) \cdot C$$


$$X = \overline{AB}$$

$$= \bar{X} \cdot C + X \cdot \bar{C}$$

$$F_1 = A \cdot B \oplus C \rightarrow$$

For (ii) $F_2 = A \oplus B \oplus C.$

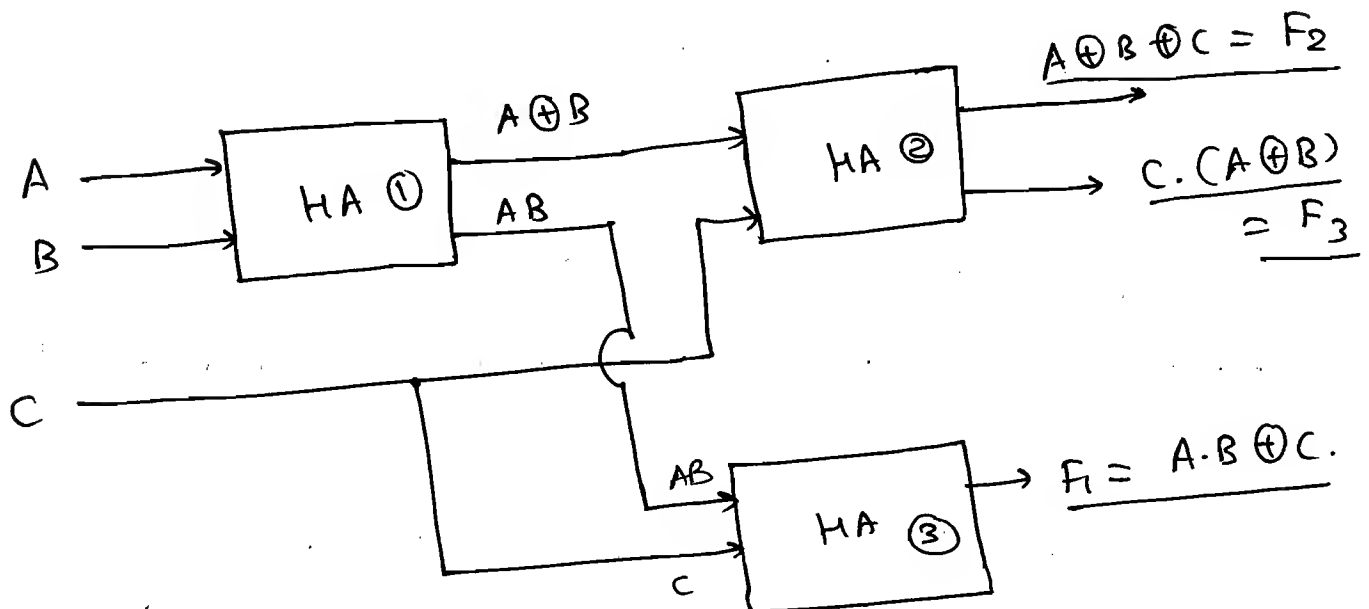(iii) $F_3 = (\bar{A}B + A\bar{B})C = C \cdot (A \oplus B)$



* Binary Address:

(1) Parallel binary Adder:

(2) Carry Look Ahead Adder:

(3) Serial Adder.

(1) Parallel binary Adder: (4 bit):


→ ~~IC = 74LS83~~

[IC = 74LS83]

$$\begin{array}{r}
 A = A_4 \ A_3 \ A_2 \ A_1 \\
 + \ B_4 \ B_3 \ B_2 \ B_1 \\
 \hline
 C_5 \ S_4 \ S_3 \ S_2 \ S_1
 \end{array}$$

$\xrightarrow{\text{FA}}$
 $\xrightarrow{\text{HA (OR) FA}}$

~~IC = 74LS83~~ + 3 FA + 1 HA (OR)
4 FA

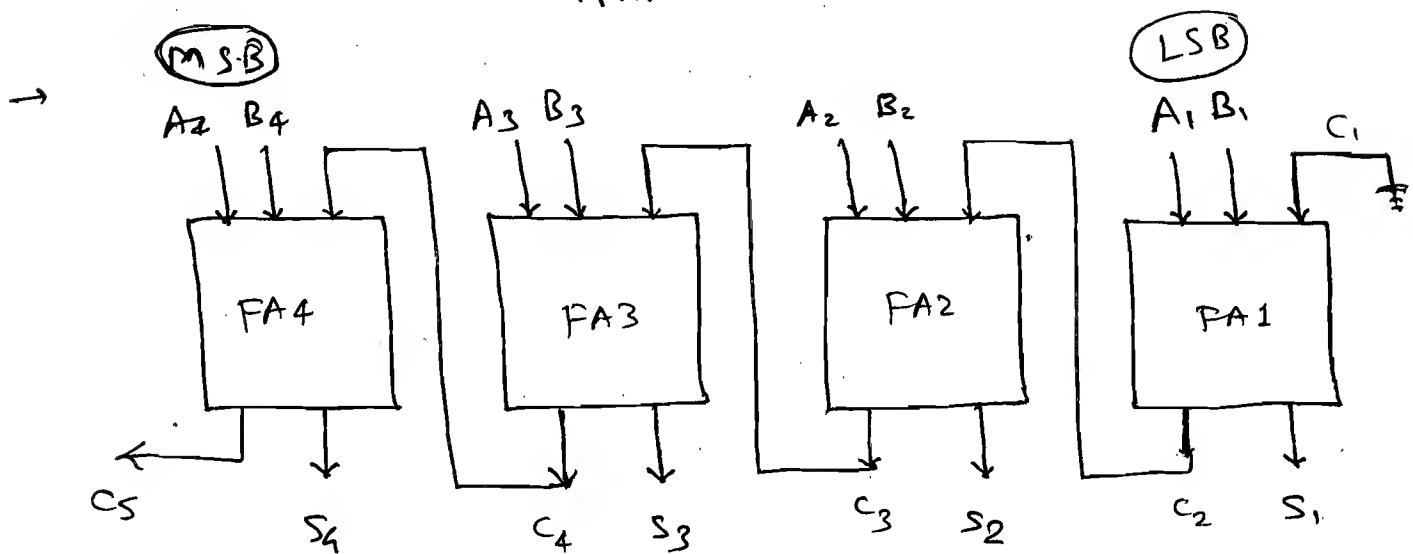

Q: how many HA required to implement 4-bit parallel adder

Ans: 7 HA &
3 OR gate

Q.

→ In a 4 bit parallel binary adder a FA takes 32 ns to produce the sum and 14 ns to produce the carry. Determine
 (i) Time required for addition.
 (ii) the addition rate of the adder.

Ans:

a)

Time required for Addition in N-bit parallel adder = $T = (N-1)t_c + \max(t_s, t_c)$.

$$\Rightarrow T = (4-1)14 + \max(32, 14).$$

$$= 42 + 32$$

$$T = 74 \text{ ns}$$

b)

$$\text{Addition Rate} = \frac{1}{T} = \frac{1}{74 \times 10^{-9}} \text{ Hz.}$$

→ This can be used upto 4 bit.



→ Disadvantages:

→ as the size of the Adder increases the Speed operation decreases as the carry

✓ has to propagate through all the FAs to overcome this we use Carry Look ahead Adder.

(2) Carry Look Ahead Address:

→ Principle:

  

$$\rightarrow C_{i+1} = C_i (A \oplus B) + AB$$

$$P_i = A \oplus B = \text{Propagation of carry}$$

$$C_i = AB = \text{Carry generation}$$

$$\therefore C_{i+1} = C_i P_i + C_i$$

$$\rightarrow \boxed{C_2 = C_1 P_1 + C_1} \quad - \textcircled{1}$$



$$\rightarrow C_3 = C_2 P_2 + C_2$$

$$\boxed{C_3 = C_1 P_1 P_2 + C_1 P_2 + C_1} \quad - \textcircled{2}$$

$$\rightarrow C_4 = C_3 P_3 + C_3$$

→ $C_4 = C_1 P_1 P_2 P_3 + C_1 P_2 P_3 + C_2 P_3 + C_3$ — (3) 73

*

  

→ In Carry Look-Ahead time taken to generate the carries C_2, C_3, C_4 is same as they are implemented by 2 level Logic.


* Advantage:

→ Its Speed of operation is very high and doesn't depend on the size of the adder.

* Disadvantage:

→ It has more hardware complexity. To overcome this we use carry look ahead generator IC.

⇒ Carry Look Ahead generator IC

 

Carry Look Ahead Adder

$$S_i = A_i \oplus B_i \oplus C_i$$

$$S_i = P_i \oplus C_i$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$



$$S_3 = P_3 \oplus C_3$$

$$S_4 = P_4 \oplus C_4$$

(3) Serial Adder: (sequential CKT)


75

→

   $T = CLK \text{ period}$

Time for 4-bit serial addition = $4T$

* 4-bit Parallel Adder/Subtractor

 

(1) If $x=1 \Rightarrow$ Ex-OR gate \rightarrow Inverters

$\rightarrow A + 1's \text{ Comp of } B + (C_1=1)$

$\rightarrow A + (2's \text{ Comp of } B)$

$\Rightarrow A - B \rightarrow$ Binary Subtraction

(2) If $x=0 \Rightarrow$ Ex-OR gate \Rightarrow Buffer

$\rightarrow A + B + (C_1=0)$

$= A + B \rightarrow$ Binary Adding

Ex-1 Determine the f^n of the above 77 circuit if the inputs are as given below:

④ $x=1$; $A = \text{Ex-3 code}$; $B = 0011 \Rightarrow \text{Function} = ?$

$$\begin{aligned} \Rightarrow A - B &= \text{Ex-3} - 0011 \\ &= \text{Ex-3} + (1100) + 1 \\ &= \text{BCD code.} \end{aligned}$$

Ex-3 to BCD code converter.

\therefore let, $\text{Ex-3} \xrightarrow{\text{of 4}} 0111 \Rightarrow 0100 \rightarrow \text{BCD}$

\uparrow
Ex-3

$$\begin{array}{r} \begin{array}{cccc} 1 & 1 & 1 & \\ 0 & 1 & 1 & 1 \end{array} \\ + \begin{array}{cccc} 1 & 1 & 0 & 0 \\ & & & 1 \end{array} \quad (\because C=1) \\ + \\ \hline \textcircled{\times} \quad \underline{0 \quad 1 \quad 0 \quad 0} \Rightarrow 4_{10} = (0100)_{\text{BCD}} \end{array}$$

\Updownarrow

⑥ $x=1$, $A = 1001$; $B = \text{BCD} \Rightarrow \text{Function} = ?$

Ans: $A = 1001$, let, $B = \text{BCD of 3}$
 $B = 0011$.

$$\begin{array}{r} \begin{array}{cccc} & 1 & & \\ A & 1 & 0 & 0 & 1 \\ + & 1 & & & \\ \hline & 1 & 1 & 0 & 0 \\ + & & & & 1 \\ \hline 1 & 0 & 1 & 1 & 0 \end{array} \end{array}$$

$= 6_{10}$ which is 9's comp. of 3_{10}

\therefore So, BCD to 9's Comp. of BCD.

$$A + 1's \text{ comp of } B + C_1 = 1.$$


$$= A + (2's \text{ comp of } B).$$

$$= A - \text{BCD.}$$

$$= 9_{10} - \text{BCD}$$

$$= 9's \text{ complement of BCD.}$$

(C)

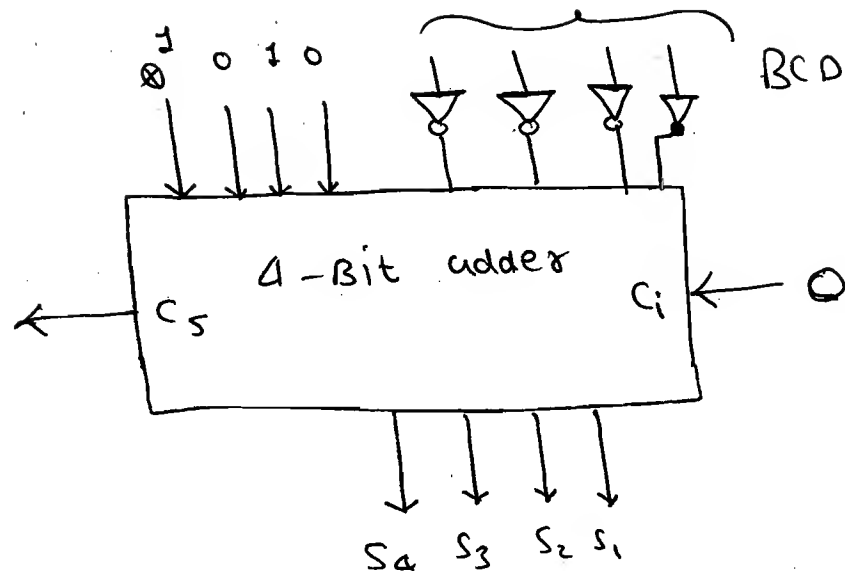

$$\Rightarrow 1010 + 1's \text{ Comp. of } BCD \quad \boxed{C_i = 0}$$

$$= \cancel{1001} + 1 + 1's \text{ Comp. of } BCD$$

$$\Rightarrow 1001 + 2's \text{ Comp. of } BCD.$$


$$= 9_{10} - BCD.$$

→ 9's Complement of CK .

NOTE: The above 9's Complement CK can be converted to a 10's Complement either by choosing $C_i = 1$ (or) by choosing

A value as $A = 1011$

* BCD Adder

 


* Output is invalid BCD if


$$S_4 S_3 S_2 S_1 > 9 \text{ (or) } C_5 = 1.$$

$S_2 S_1$	00	01	11	10
$S_4 S_3$				
00				
01				
11	1	1	1	1
10			1	1

→ i.e. output is invalid if

$$Y = S_4 S_3 + S_4 S_2 + C_5.$$

 

 


→ Hence, one BCD adder requires ^{two} 4-bit parallel adders

* Ex-3 Adder

(1) If $C_5 = 1 \Rightarrow$ Add $\begin{array}{ccc} \bar{C}_5 & \bar{C}_5 & C_5 \\ 0 & 0 & 11 \end{array}$

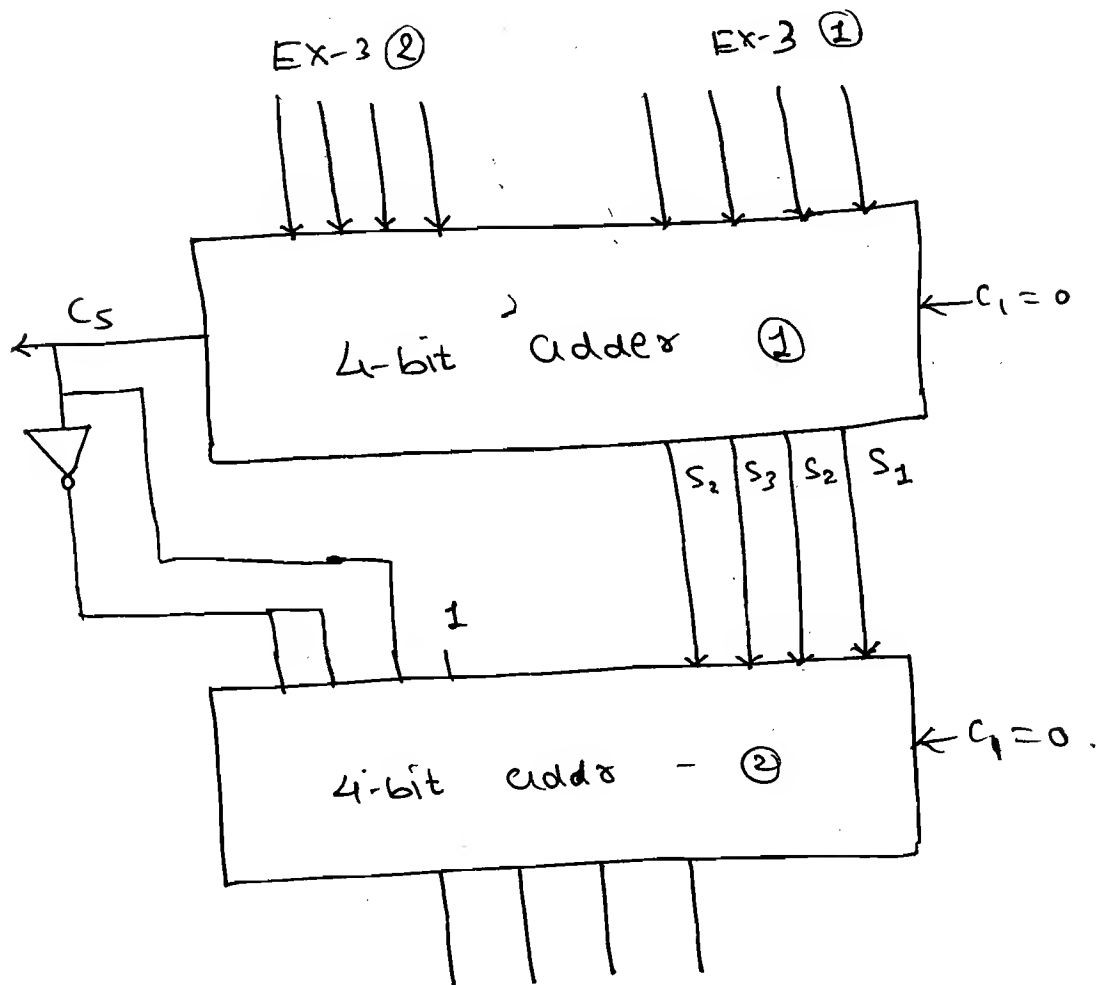(2) If $C_5 = 0 \Rightarrow$ Subtract 0011
 $=$ Add 2's Comp of 0011
 $=$ Add $\begin{array}{ccc} \bar{C}_5 & \bar{C}_5 & C_5 \\ 1 & 1 & 01 \end{array}$



* 2-Bit Magnitude Comparator:

→ The truth table of n bit magnitude comparator is not preferred for the design as the no. of rows in the table is 2^{2n} .

n -bit Mag Comparator \rightarrow No. of rows = 2^{2n}
 $= 2^{2n}$



*Q → How many possible way in 2 bit mag. comparator that $A > B$?

Ans:


$A_2 A_1$	$B_2 B_1$	
0 0	—	
0 1	0 0	\rightarrow ①
1 0	0 0 0 1	\rightarrow ②
1 1	0 0 0 1 1 0	\rightarrow ③

So, 6 possibility that $A > B$.

*

  


 - ① $A=B$ if $A_2=B_2$ and ~~$x_2=1$~~ $A_1=B_1$ 83
i.e. $A=B$ if $x_2=1$ and $x_1=1$.
i.e. $A=B$ if $x_1 \cdot x_2 = 1$.



- ② $A > B$ if $A_2 > B_2$ (or) $A_2 = B_2$ and $A_1 > B_1$.
i.e. $A > B$ if $A_2 \bar{B}_2 + x_2 \cdot A_1 \bar{B}_1 = 1$ — ②
- ③ $A < B$ if $A_2 < B_2$ (or) $A_2 = B_2$ and $A_1 < B_1$.
i.e. $A < B$ if $\bar{A}_2 B_2 + x_2 \cdot \bar{A}_1 B_1 = 1$ — ③

 * Odd parity generator and parity checker.




P is chosen so that
 $A, B, C, P \rightarrow$ odd parity.

$F = 1$ if even parity
 $F = 0$ if odd parity
 occurs for A, B, C, P .

\rightarrow odd parity generator:

A	B	C	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$P(A, B, C) = \sum m(0, 3, 5, 6)$$

 

$$P = A \oplus B \oplus C$$

(or)

$$P = A \odot B \oplus C$$

A	B	C	P	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$F = \sum m(A, B, C, P)$$

$$= \sum m(0, 3, 5, 6, 9, 10, 12, 15)$$

	C	00	01	11	10
A	B				
0	0	1		1	
0	1		1		1
1	0	1		1	
1	1		1		1


* All minterms have
Even no of 0's.

$$\Rightarrow F = A \oplus B \oplus C \oplus P$$

* Decoder:

→ It converts the binary information on i/p lines to one or many o/p lines.

→ n to m decoder = (1 out of m decoder).

 


$E=0 \Rightarrow$ Decoder is enabled


$E=1 \Rightarrow$ Decoder is disabled

$$m \leq 2^n$$

* 2 to 4 decoder (Active High o/p).

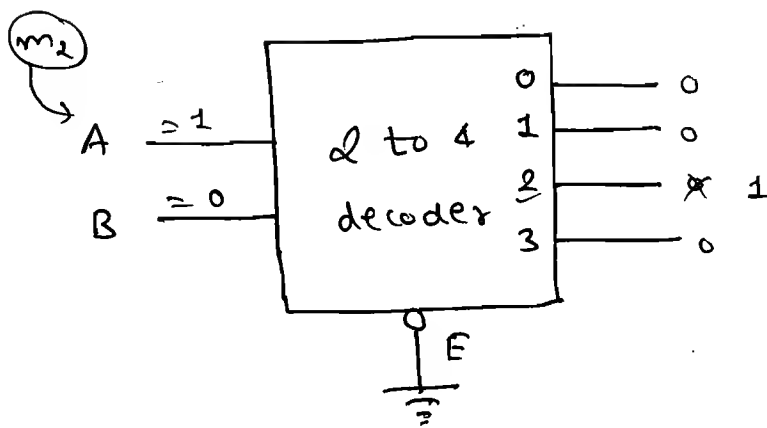


⊛ 2 to 4 decoder (Active Low o/p).

 

Most widely used in practice because it generate less noise compare to Active High Decoder.

⇒ Internal circuits:

 


* Decoders
⇒ AND, NAND gates.

Ex-1 Implement $F(A,B) = \sum m(0,2,3)$ using
 a decoder (a) with active high o/p.s
 (b) with active low o/p.s.


Ans: (a) With active high o/p.

A	B	F
0	0	1
0	1	0
1	0	1
1	1	1

m_0
 m_2
 m_3

 

(b) With active low o/p.

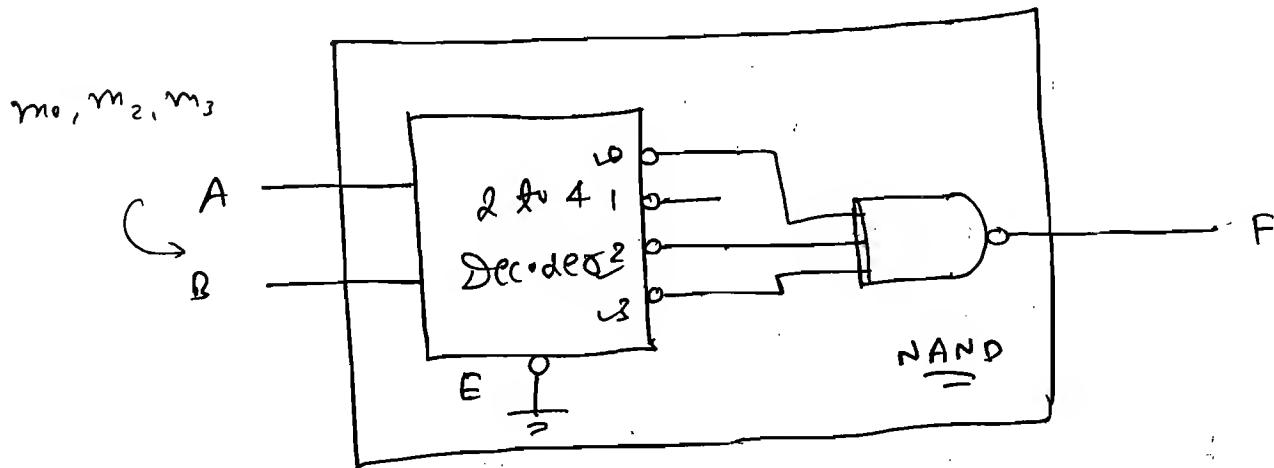


Ex-2 Implement a full Subtractor using a decoder with active Low outputs.

Ans:

$$D(A, B, b_i) = \sum m(1, 2, 4, 7).$$

$$B(A, B, b_i) = \sum m(1, 2, 3, 7).$$

 


Ex-3 How many 2 to 4 decoder required to construct 1 out of 32 decoder.

Ans: Short cut:

Required No. of O/P	Given no. of o/p	No. of Decoders
$\frac{32}{4} = 8$		8
$\frac{8}{4} = 2$		+ 2
$\frac{2}{4} = 0.5 \approx 1$		+ 1
		<u>11</u>



3 levels.

⇒

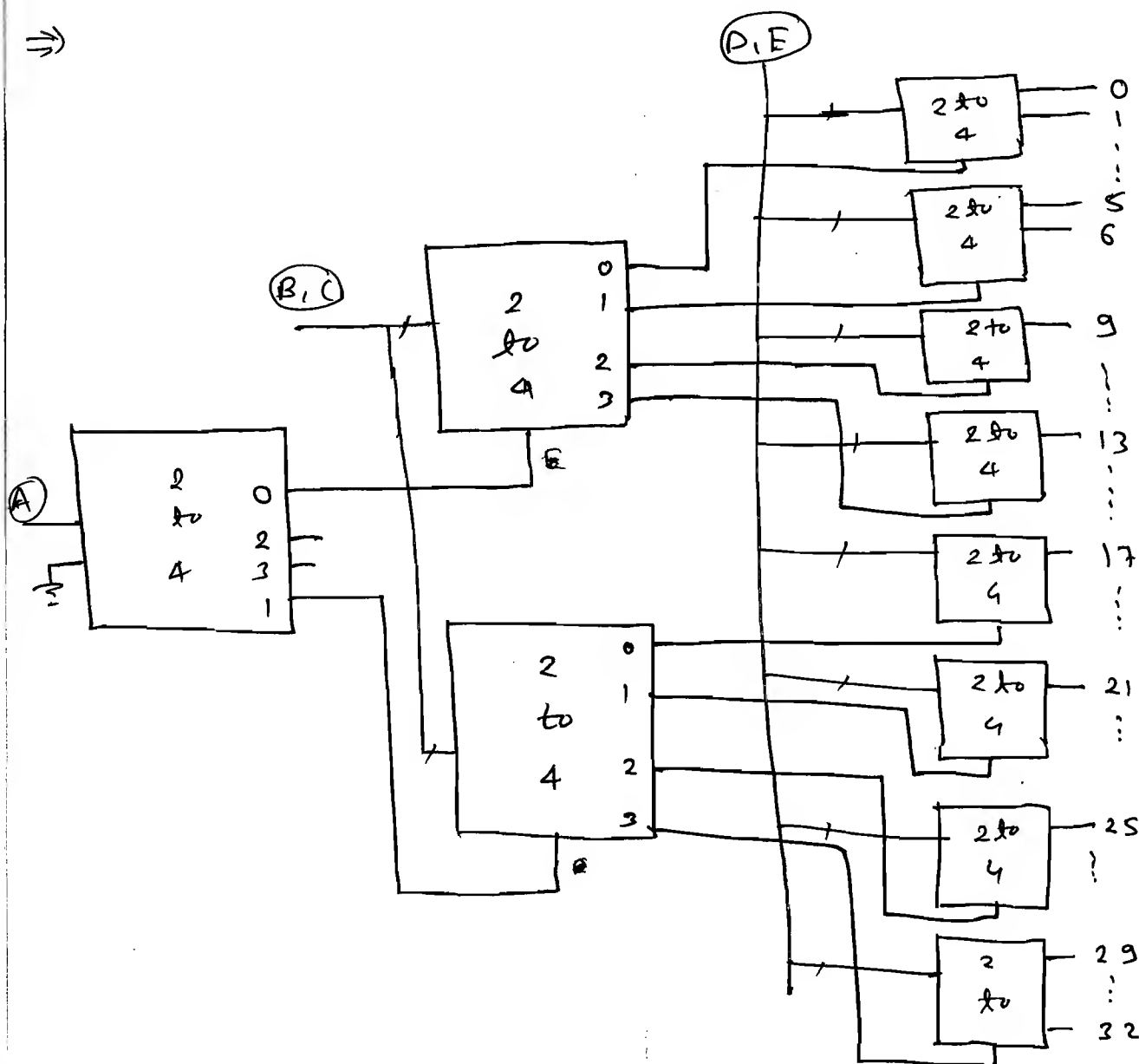

* Demultiplexer (one to many ckt, Serial to parallel converter). 91

1:4 Demux

  

→ A Demux is similar to a decoder.

→ A 1:4 Demux is converted to a 2 to 4

Decoder by making two changes.

(1) selection of Demux are converted to the I/Os of 2 to 4 decoder.

[illegible]

1
2
3


•

(

 (

 (

(
(
(

 

CC

$$A = 0_4 + 0_5 + 0_6 + 0_7.$$

$$B = 0_2 + 0_3 + 0_6 + 0_7.$$


$$C = 0_1 + 0_3 + 0_5 + 0_7.$$

NOTE:

→ The encoder follows the OR Logic.

→ The limitation of encoder is it can't perform the coding if more than 1 input is active simultaneously. To overcome this, we use priority encoder.

* Priority Encoder:

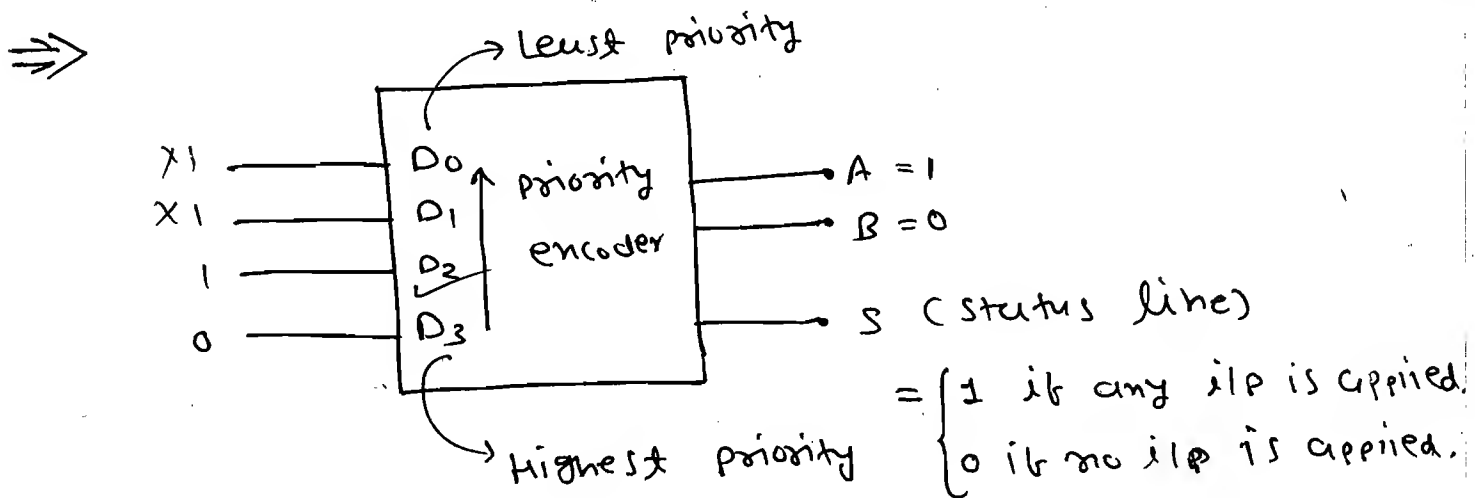

⇒

	D_3	D_2	D_1	D_0	A	B	S
$m_0 \leftarrow$	0	0	0	0	0	0	0
$m_1 \leftarrow$	0	0	0	1	0	0	1
$m_2, m_3 \leftarrow$	0	0	1	X	0	1	1
$m_4 \text{ to } m_7 \leftarrow$	0	1	X	X	1	0	1
$m_8 \text{ to } m_{15} \leftarrow$	1	X	X	X	1	1	1

(b) Priority Encoder table.

$$\rightarrow B(D_3, D_2, D_1, D_0) = \sum m(2, 3, \cancel{4}, \cancel{5}, \cancel{6}, \cancel{7}, 8, 9, 10, \dots, 15).$$

		$D_1 D_0$			
		00	01	11	10
$D_3 D_2$	00			1	1
	01				
	11	1	1	1	1
	10	1	1	1	1

$$B = D_3 + \overline{D_2} D_1$$

$$\rightarrow A(D_3, D_2, D_1, D_0) = \sum m(4, 5, 6, 7, \dots, 15).$$

		$D_1 D_0$			
		00	01	11	10
$D_3 D_2$	00				
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$A = D_2 + D_3$$

$$\rightarrow S = \sum m(1, 2, 3, \dots, 15).$$

		$D_1 D_0$			
		00	01	11	10
$D_3 D_2$	00	1	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$\therefore S = \overline{D_3} + \overline{D_2} + \overline{D_1} + \overline{D_0}$$

$$S = D_3 + D_2 + D_1 + D_0$$

NOTE:

74LS138 \Rightarrow $\begin{cases} 3 \text{ to } 8 \text{ decoder} \\ (\text{Active low outputs}) \end{cases}$


74LS148 \Rightarrow $\begin{cases} 8\text{-input, 3-output} \\ \text{priority encoder} \end{cases}$

* Multiplexer:

(Many to one circuit,
parallel to serial converter).

*

4:1 MUX.

 

\therefore

A	B	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

\Rightarrow 4:1 MUX $\Rightarrow F = \bar{A}\bar{B}I_0 + \bar{A}BI_1 + A\bar{B}I_2 + ABI_3$

$$\therefore F = m_0 I_0 + m_1 I_1 + m_2 I_2 + m_3 I_3.$$

* E.g.: Given $I_0 = I_1 = 1$; $I_2 = I_3 = 0$.

$$\therefore F = m_0 \cdot 1 + m_1 \cdot 1 + 0 + 0.$$

$$\therefore F = m_0 + m_1$$

$$\therefore F = \sum m(0, 1).$$


Ex-1 Implement the Sum of half Adder using 4:1 MUX.

Ans:

$$S(A, B) = \sum m(1, 2).$$

$$S(A, B) = m_1 + m_2$$

 
Choose $I_1 = I_2 = 1$ &
 $I_0 = I_3 = 0$



Ex-2 Which of the following is implemented by the following mux.

- (a) Sum output of Full adder.
- (b) Carry output of Full adder.
- (c) Difference output of Full Subtractor.
- ✓ (d) Borrow output of Full Subtractor.


Q Sum of 8:1 MUX

 

$$F = \sum m(1, 2, 3, 7)$$

Ex-2 What are the Logic gates represented by the following mux circuits.

Q

 

$$F = m_0 C + m_1 C + m_2 \bar{C} + m_3 \bar{C}$$

$$F = (\bar{A}\bar{B} + \bar{A}B)C + (A\bar{B} + AB)\bar{C}$$

$$F = \bar{A}C + B\bar{C}$$

$$F = (\bar{A}B + A\bar{B})C$$

$$F = \bar{A}B + A\bar{B}$$


$$F = (\bar{A}B + A\bar{B})C + (A\bar{B} + AB)\bar{C}$$

$$= \bar{A}C + A\bar{C}$$

$$F = A \oplus C$$

∴ Ex-OR gate

(b)

 

$$\therefore F_1 = m_0 = \bar{x}_1$$

$$\therefore F_1 = \bar{x}_1$$


$$\therefore F = F_1 \bar{x}_2 + x_2 x_1$$

$$= \bar{x}_1 \cdot \bar{x}_2 + x_2 x_1$$

$$\therefore \boxed{F = x_1 \oplus x_2}$$

Ex-4 Determine the output of the following MUX.

Ans.

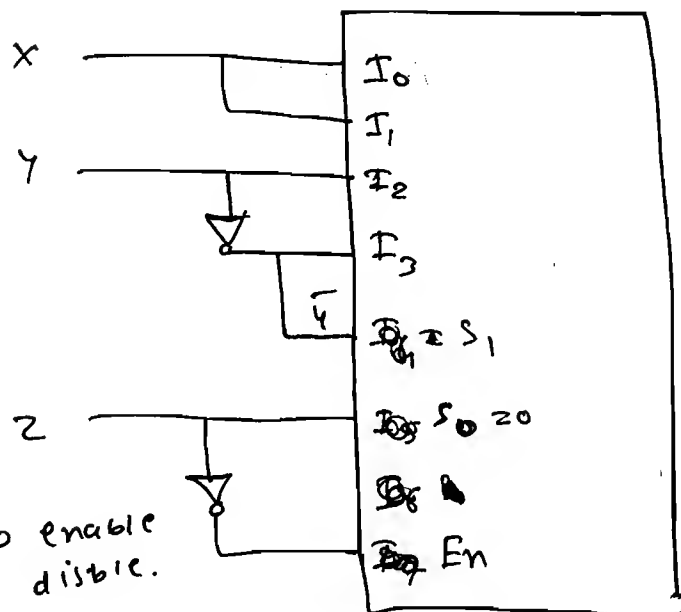

$Z=0$ enable
 $Z=1$ disable.

$$F = (m_0 + m_1) X$$

$$+ m_2 Y + m_3 \bar{Y}$$

$$= (\bar{S}_1 \bar{S}_0 + \bar{S}_1 S_0) X$$

$$+ S_1 \bar{S}_0 Y + S_1 S_0 \bar{Y}$$

$$= \bar{S}_1 X + S_1 \bar{S}_0 Y + S_1 S_0 \bar{Y}$$

$$= \bar{S}_1 X + S_1 Y + 0$$

$$= XY + 0$$

$$= XY$$

\Rightarrow

$$F = x \cdot y \cdot \bar{z}$$

 $\Rightarrow z=0 \rightarrow \text{enable.}$
 $z=1 \rightarrow \text{disable.}$

Ex-5 How many 4:1 mux required to construct 128:1 MUX.

Ans: $\frac{\text{Required No. of Inputs}}{\text{Given No. of I/P}}$


$$= \frac{128}{4} = 32 \xrightarrow{\text{No. of MUX}} 32$$

$$\therefore \frac{32}{4} = 8 \xrightarrow{+}$$


$$\frac{8}{4} = 2 \xrightarrow{+2}$$

$$\frac{2}{4} = 0.5 \xrightarrow{+1}$$

$$\underline{43}$$

 

 (b) $2:1$ MUX $\longrightarrow 2^n:1$ MUX.



So, $\boxed{2^n - 1}$ $2:1$ MUX required for $2^n:1$ MUX.

Ex-5 How many $2:1$ MUX are req. to realize

- (a) AND gate
- (b) OR gate
- (c) EX-OR gate.

Ans:

$$F = \bar{A}I_0 + AI_1$$


$$F = AB$$

$$F = AB + 0 \cdot \bar{A}$$

$$F = 0 \cdot \bar{A} + B \cdot A$$

$$F = \bar{A}I_0 + AI_1$$

So, $I_0 = 0$, $I_1 = B$.

 

⑥ OR gate:

$$\therefore F = \bar{A}I_0 + A I_1$$


$$F = A + B.$$

$$= A + \bar{A}B$$

$$F = \bar{A}B + A \cdot 1.$$


$$\therefore F = \bar{A}I_0 + A \cdot I_1$$

 \therefore So, Choose $I_0 = B, I_1 = 1.$




⑦ Ex-or gate:
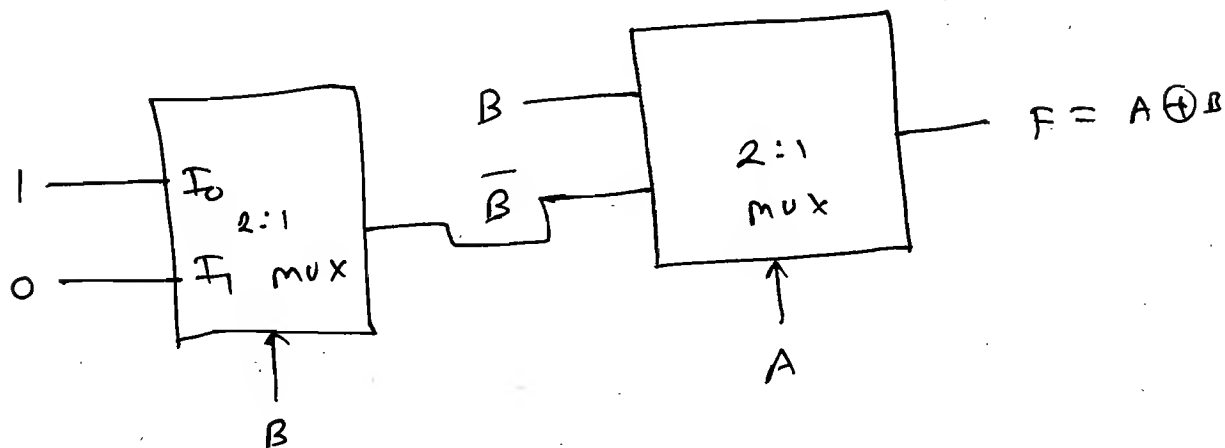
$$\rightarrow F = \bar{A} \underset{\substack{\uparrow \\ I_0}}{B} + A \underset{\substack{\uparrow \\ I_1}}{\bar{B}} = A \oplus B.$$



Ex-6 Implement $F(A, B, C, D) = \sum m(0, 1, 3, 5, 6, 10, 11, 13, 14)$ using 4:1 MUX.

Ans:

 

Method - 1

AB =		00	01	10	11
		I_0	I_1	I_2	I_3
00	$\bar{C}\bar{D}$	(0)	4	8	12
01	$\bar{C}D$	(1)	(5)	9	(13)
10	$C\bar{D}$	2	(6)	(10)	(14)
11	CD	(3)	7	(11)	15
		$\bar{C}\bar{D} + \bar{C}D + CD$ $= \bar{C} + D$	$C\bar{D}$	C	$C \oplus D$

Method :- 2

If A, B are selection line

		CD				
		00	01	11	10	
AB	00	1	1	1		$\rightarrow I_0 = \bar{C}\bar{D} + \bar{C}D + CD = \bar{C} + D$
	01		1		1	$\rightarrow I_1 = \bar{C}D + C\bar{D} = C \oplus D$
	10		1	1	1	$\rightarrow I_2 = \bar{C}D + C\bar{D} = C \oplus D$
	11			1	1	$\rightarrow I_3 = CD + C\bar{D} = C$

→ NOTE: If C & D are selection lines

103


CD \ AB	00	01	11	10
00	1	1	1	
01		1		1
11		1		1
10			1	1

$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$
 $I_0 = \bar{A}\bar{B} \quad I_1 \quad I_2 = \bar{B} \quad I_3 = B$
 $\quad \quad \quad = \bar{A} + B$

Ex-1 $F(A, B, C) = \sum m(0, 3, 5, 6)$ using 4:1 mux.

Ans:

Method-I:

 

	I_0	I_1	I_2	I_3
\bar{A}	0	1	2	3
A	4	5	6	7
	\bar{A}	1	A	\bar{A}

Method-II (K-MAP)


BC \ A	00	01	11	10
0	1	1	1	
1		1		1

$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$
 $I_0 = \bar{A} \quad I_1 = 1 \quad I_2 = \bar{A} \quad I_3 = A$

Ex-2 In the following Mux tree, determine the

★ values of $P, Q, R, S = ?$

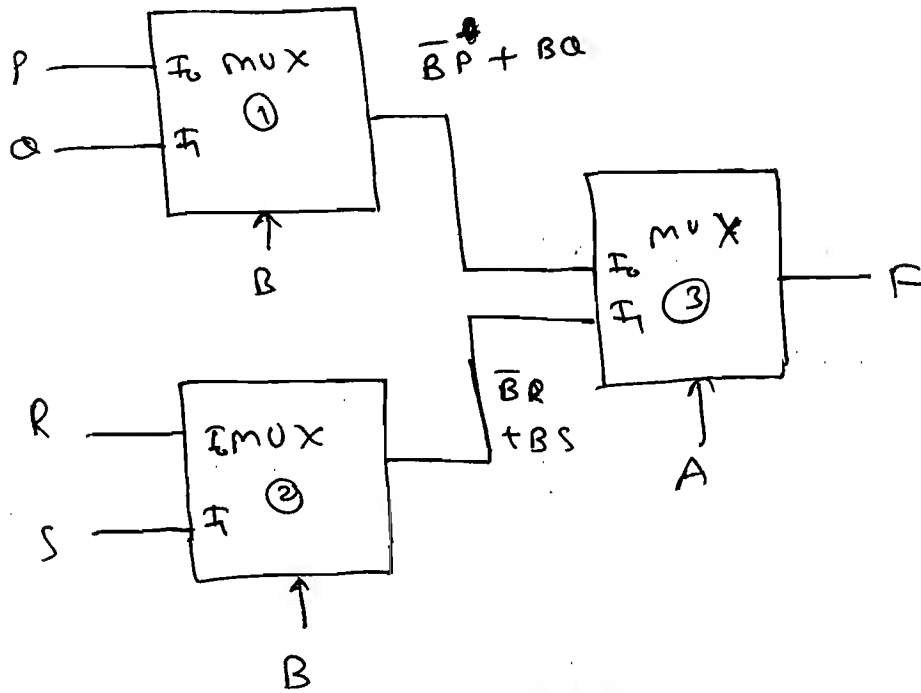Where, $F(A, B, C) = \sum m(1, 2, 4, 5, 6)$.



$$\therefore F = \bar{A} (\bar{B}P + BQ) + A (\bar{B}R + BS)$$

$$\therefore F = \bar{A}\bar{B}P + \bar{A}BQ + A\bar{B}R + ABS$$

AB		00	01	11	10
AC	0	0	1	1	1
	1	1	3	7	1

$$I_0 = C \quad I_1 = \bar{C} \quad I_2 = \bar{C} \quad I_3 = 1$$

$\nearrow \quad \nearrow \quad \nearrow \quad \nearrow$
 $P \quad Q \quad R \quad S$

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

$$\therefore F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A$$

Ex-2 Using $n=1$ MUX we can implement 205
all ' $\log_2 N$ ' variable functions and
Some of " $\log_2 N + 1$ " variable functions
[T/F].

Ans: let, 4:1 MUX


$$\text{So, } \log_2 4 = 2$$

→ True : because the other functions required
external logic gates along with MUX.

* Rom (Read only Memory).

\Rightarrow Decoder + Prog. or gates } = Rom.
(Fixed AND gates) (encoder)

 \rightarrow Rom is a Combinational circuits and we can use it to implement sum of minterms expression as shown in the following example:




$$F_1(A, B, C) = \sum m(0, 1, 6, 7).$$

$$F_2(A, B, C) = \sum m(2, 3, 4, 5).$$


$$\text{size} = 2^3 \times 2 = 16.$$

⇒

Read only memory

 

⇒

 


→ Rom size indicates that how many bits can be stored.

Ex-1 Determine the size of the Rom for the following functions.

① Rom as 3 bit binary multiplier.

②

 

$$y = 3 + 3 = 6$$

$$y = 6$$

$$\overset{111}{7}_{10} * \overset{111}{7}_1 = 49_{10}$$

$$2^y > 49$$


$$\boxed{y = 6}$$

$$\therefore \text{Rom size} = 2^x \times y = 2^6 \times 6 = 384.$$

② Rom as 4-bit squarer.

Ans:

$$x = 8$$

 

~~64~~

1111

1111

~~64~~

~~64 x 64~~

~~4 x 4~~

~~2 x 2~~

~~y = 8~~

$$\cancel{x = 4.}$$

$$\cancel{2^4 \times 8 = 16 \times 8 = 128.}$$

$$15 \times 15 = 225_{10}$$

\therefore

$$2^y > 225$$


$$\boxed{y = 8}, x = 4.$$

$$\therefore \text{size} = 2^4 \times 8 = 128.$$

* PLA (Prog. Logic Array):

109

⇒ Prog. AND gates + Prog. OR gates.

 

$$F_1(A, B, C) = A\bar{B}\bar{C} + \bar{A}B\bar{C}$$

$$F_2(A, B, C) = \bar{A}B + A\bar{C}$$

Product terms \rightarrow


$$P_1 = A\bar{B}\bar{C}$$

$$P_2 = \bar{A}B\bar{C}$$

$$P_3 = \bar{A}B$$

PLA size \Rightarrow (3 inputs, 3 product terms, 2 outputs).

 Ex-1 In the following PLA Determine the product terms P_1, P_2, P_3, P_4, P_5



$$F_1(A, B, C) = \bar{A}\bar{B}\bar{C} + A\bar{B}C + AB.$$

$$= \bar{A}\bar{B}\bar{C} + (\bar{B}C + B)A$$

$$= \bar{A}\bar{B}\bar{C} + AC + AB.$$

$$= B(\bar{A}\bar{C} + A) + AC$$

$$F_1(A, B, C) = \bar{A}\bar{B}\bar{C} + AB + AC = \bar{A}\bar{B}\bar{C} + AC$$

$$F_2(A, B, C) = \bar{A}\bar{B}\bar{C} + ABC + \bar{A}C$$

$$= \bar{A}\bar{B}\bar{C} + C(AB + \bar{A})$$

$$= \bar{A}\bar{B}\bar{C} + BC + \bar{A}B.$$

$$= \bar{A}(\bar{B}\bar{C} + B) + BC$$

$$= \bar{A}(\bar{C} + B) + BC$$

$$F_2 = \bar{A}\bar{C} + \bar{A}B + BC = \bar{A}\bar{C} + BC$$

$$F_3 = \bar{A}\bar{B}\bar{C} + BC + A\bar{B}C.$$

$$= \bar{A}\bar{B}\bar{C} + C(A + B).$$

$$= AC + BC + \bar{A}\bar{B}\bar{C}$$

$$= AC + B(C + \bar{A})$$

$$= AC + BC + \bar{A}B.$$

$$= AC + \bar{A}B.$$

$F_1 =$

	BC			
	00	01	11	10
A	0			1
1		1		1

$$F_1 = \underline{AC} + BC$$

$F_2 =$

	BC			
	00	01	11	10
A	0	1		
1			1	

$$F_2 = \bar{A}\bar{B} + BC$$

$F_3 =$

	BC			
	00	01	11	10
A	0		1	1
1		1	1	

$$F_3 = \underline{AC} + \bar{A}B$$

$\therefore P_2 = AC, P_1 = BC, P_3 = \bar{A}B$

$P_4 = \bar{A}B, P_5 = BC$ or

$P_5 = \bar{A}B, P_4 = BC$

size = (3, 5, 3)
 (input product output term)

* PAL : Prog. AND gate + fixed OR gate.

GRAL : Generic Array logic

= Prog. AND gates + fixed OR gate
 + Prog. Output Logic
 (E.g. Tri-state O/P, Normal d.p etc).

Ex-1 How many invalid 10 combinations occur at input of BCD adder?

Ans: - No. of Invalid BCD combinations at Input.


= Total Input combinations
- No. of Valid combinations.

$$= (16 \times 16) - (10 \times 10) \\ = 156.$$

* Overflow:

- overflow is used in signed arithmetic.
- overflow occurs whenever the result exceeds the range of signed no.s.
- The overflow condition can be verified by the following methods:

①

 

If $x=1$ and $y=0$ (or) $x=0$ and $y=1$ } overflow occurred.



② Overflow occurs if 2 +ve no.s are added the result is -ve or 2 -ve no.s are added the result is +ve.

E.g. Consider 2's comp. nos.

① $\begin{array}{r} x=0 \\ y=1 \end{array} \begin{array}{r} \text{---} \\ \text{---} \end{array}$

$$\begin{array}{r} 1 \ 0 \ 1 \ (-3) \\ + \ 1 \ 1 \ 0 \ (-2) \\ \hline 0 \ 1 \ 1 \end{array}$$

Overflow occurred (or)

Two -ve nos are added result is +ve

② $\begin{array}{r} y=0 \text{---} \end{array}$

$$\begin{array}{r} 0 \ 1 \ 0 \ (2) \\ + \ 0 \ 1 \ 1 \ (3) \\ \hline 1 \ 0 \ 1 \ (-3) \end{array}$$

Overflow occurred (or)

Two +ve nos are added result is -ve

③ $\begin{array}{r} y=1 \text{---} \end{array}$

$$\begin{array}{r} 1 \ 1 \ 0 \ (-2) \\ + \ 1 \ 1 \ 0 \ (-2) \\ \hline 1 \ 0 \ 0 \ (-3) \end{array}$$

No overflow

Ex-1

$$\begin{array}{r} x \\ + \ y \\ \hline z \end{array}$$

overflow

If $x=1, y=1$ but $z=0$ (or)


$x=0, y=0$ but $z=1$

Expression for overflow

$$\bar{x} \cdot \bar{y} \cdot z + x \cdot y \cdot \bar{z}$$

★ Sequential Circuits: (1 bit memory elements)


⇒ * S-R Latch:

 

S	R	Q
0	0	No change
0	1	0
1	0	1
1	1	Indeterminate state

($\because Q = \bar{Q} = 0$).


⇒

 

*

S	R	Q
0 1	0 1	<div style="border: 1px solid black; padding: 2px;">1</div>
0 0	0 0	1

 
Ex-1 In the following X-Y Latch initially $x=1$ & $y=1$. Determine the outputs P & Q. If the Y input is change as 0,1,0,1,0,1,....



so, P is fixed at $P=0, Q=1$.

1 = X
0 = Y
1 = Y
0 = Y

 Ex-2 In the following X-Y Latch the seq. of inputs are $xy = 01, 00$ and 11 - determine the values of P & Q.



10, 11, 00.




10, 11, 00.

X	Y	PQ
0	1	10
0	0	11
1	1	01 (or)
		00

01 ← If Gate 1 is faster than Gate 2.
00 ← If Gate 2 is faster than Gate 1.

* Clocked S-R flip flop:

   → Synchronized latch is called flip-flop.



$T =$ Clock period

$\frac{1}{T} = f =$ Clock freq.

* Truth table:



117

S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Ambiguous state

do not apply.

* Characteristic Table:

S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

  


$$Q(t+1) = S + \bar{R}Q(t)$$

* Clocked D-bip flop:

→ used in shift Register

→ D → Data, Delay.

 

* Truth Table:

D	Q(t+1)
0	0
1	1

Annotations: A circle with 'S=0, R=1' has an arrow pointing to the row where D=0. Another circle with 'S=1, R=0' has an arrow pointing to the row where D=1.


* Characteristic table:

D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1


* Characteristic equation:

$$Q(t+1) = D$$

* Clocked J K - Flip Flop.

 

(0/2)

 

* Truth table:


S	R	$Q(t+1)$
J	K	
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

* Characteristic Table:

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


Logic

* Characteristic Equation:

 


$$\therefore Q(t+1) = J \cdot \overline{Q(t)} + K \cdot Q(t)$$

*

 

* Clocked J-Flip-Flop:

 

* Truth Table:

T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

* Characteristic Table:


T	$Q(t)$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

$\left. \begin{matrix} 0 \\ 1 \end{matrix} \right\} Q(t)$
 $\left. \begin{matrix} 1 \\ 0 \end{matrix} \right\} \overline{Q(t)}$


* Characteristic eqⁿ:

$$Q(t+1) = T \oplus Q(t)$$



Q

 

Q

 

  * Asynchronous (or) Direct Inputs → Preset (Pr), Clear (Cr).



CLK	Pr	Cr	Q
0	0	1	1
0	1	0	0
1	1	1	depends on FF I/p.

* Setup, Hold times of FF.



(1) Setup time:

→ It is the minimum time by which the Input should come ahead of the clocked input.

  (2) Hold time:

→ It is the minimum time for which the input should be maintained constant after applying the clock pulse.


→ If setup time and hold times are not satisfied then the FF enters into metastable state i.e. neither zero nor '1' output.



* Propagation Delay for FF.


→ It is the time taken by the flip flop to change its state.

(c) (i.e. from L → H (or) H → L.)

 


$$t_p = \frac{t_{PLH} + t_{PHL}}{2}$$

(b)

 

*

 


→ For proper FF operation

$$t_{Hd} < t_{PLH}, t_{PHL}$$


* Types of Triggering:

1) Level Triggered FF

 


2) Edge Triggered FF:

 (a) Positive Edge Triggered FF
(Leading Edge Triggered FF).




 (b) Negative Edge Triggered FF
(Trailing Edge Triggered FF).



* Determine the o/p freq. of following FF if the CLK freq is 5 kHz.

(u)

 

NOTE:


→ If a FF is in toggle mode the o/p freq is half of the CLK freq. with 50% duty cycle. (i.e) A toggle mode FF will act as freq. divider by 2.

→ $J = K = 1 \Rightarrow$ FF is in Toggle.

i.e.

$$Q(t+1) = \overline{Q(t)}$$

CLK	Q
0	0
1	1
2	0
3	1
4	0

 


$$T_o = 2T$$

$$\frac{1}{T_o} = \frac{1}{2T} \Rightarrow$$

$$f_o = \frac{f}{2}$$


$$\therefore f_o = 2.5 \text{ kHz.}$$

(b)

 

CLK	Q	\bar{Q}
0	1	0
1	0	1
2	1	0
3	0	1
4	1	0

→

 


$$T_0' = 2T$$

$$\therefore f_0 = 2.5\text{ kHz}$$

(c)

* method - (1)

 

* method - (2) ✓

→ D-FF char. eqn $\Rightarrow Q(t+1) = D$ — (1)

But $D = \bar{Q}(t)$ — (2)

put (2) in (1)

$$\therefore Q(t+1) = \bar{Q}(t)$$

FF is in "toggle mode"



hence $f_0 = \frac{f}{2}$

$$\therefore f_0 = 2.5 \text{ kHz}$$

* Race Around Condition: (RAC).

→ RACE AROUND CONDITION occurs in Level
trigger bip flop and doesn't occur in
edge triggered FFs.

  → $\Delta t = \text{FF prop. delay} \approx 2\text{ns}$



⇒ "RAC" is when $J = K = 1$ and $t_p \gg \Delta t$.

→ Output Toggles many times instead of once.

* How to avoid RAC (in level triggered FF).


① Choose FF prop delay ' Δt ' such that.

$$t_p < \Delta t < T.$$

② Master-Slave JK FF.

* Master slave JK FF

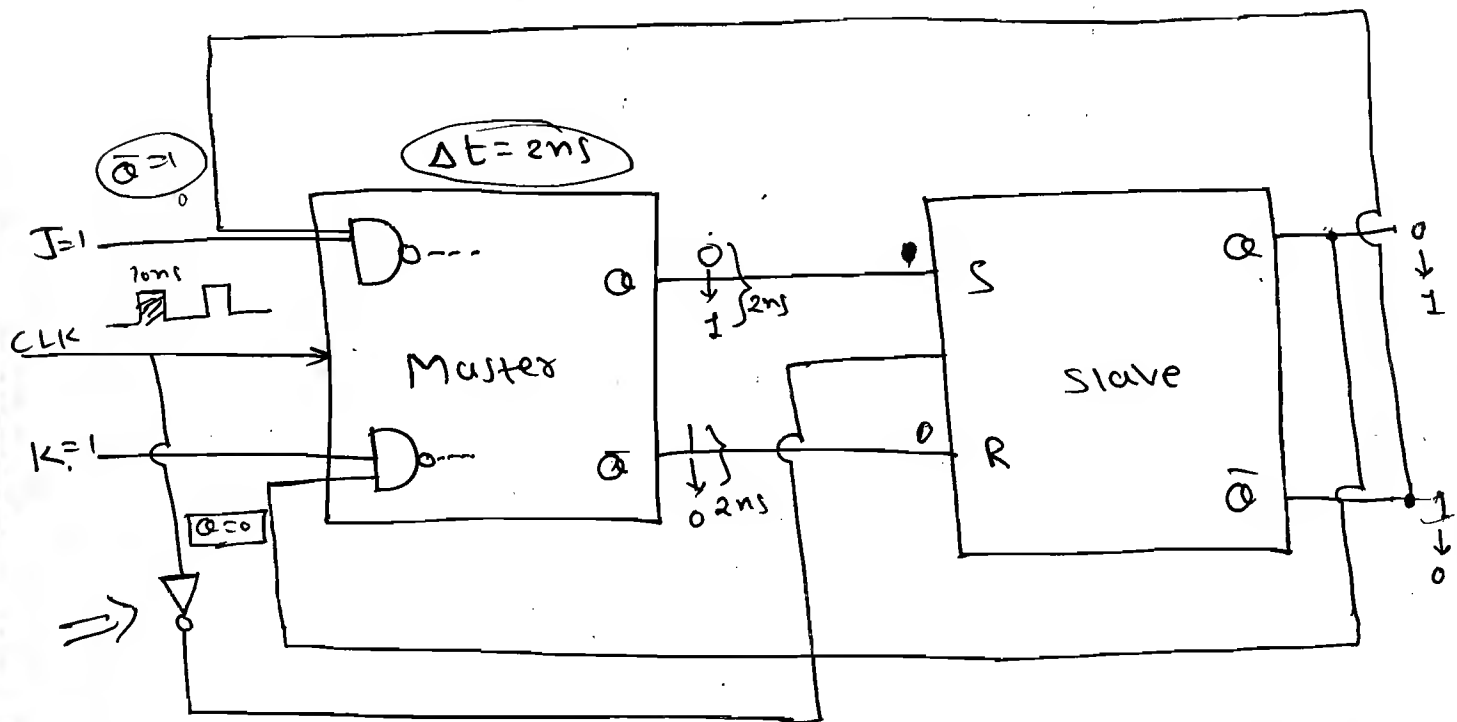→ In master slave JK FF the feedback values @ and \bar{Q} do not change during the clock pulse. Even though the output changes. Hence, 'RAC' doesn't occur.




→ In master slave J-k flip flop the feedback values 0 and \bar{Q} do not change during the clock pulse because they are taken from inactive slave FF. Hence 'RA' doesn't occur.

→ Master Slave JK FF output is similar to the negative edge triggered JK flip flop

Ex-1 In a master slave D flip flop Draw 131


The clk of master and slave is the clock and D inputs are as given below.

 → Master is active and $Q_{\text{master}} = 0$



→ Slave clk is similar to -ve Edge Triggered FF clk.

 NOTE: Master slave JK FF as JKFF as Positive Edge triggered FF.



→ In slave we can use J-K flip flop
instead of S-R flip flop. But is more
costly than S-R.





① Shift Register → "Sequential memory".

② Counters


Ⓐ to count the no. of pulses.


Ⓑ Frequency Divider.

* 3-Bit Shift Register:

    



① Serial in Parallel out =

 

 

* 'N' Bit Shift Register.
 'N' clock pulses. $\text{time} = N \cdot T$ sec.

② Serial in serial out:

  


$N + (N-1) = (2N-1)$ CLK. periods.

$$\text{time} = (2N-1) T.$$

$N = \text{No. of FF.}$

③ Parallel in parallel out:


$P_2, P_1, P_0 = \text{Parallel input}$

 

→ No clock pulse is required.

→ Preset is asynchronous input therefore no clock pulse is required.

④ Parallel in Serial out:

 

⇒ $\boxed{\text{Time} = (N-1)T}$

Input

P_2	P_1	P_0
1	0	1

$Q_2 = 1, Q_1 = 0, Q_0 = \phi$

after 1 CLK.

$Q_2 = 1, Q_1 = 1, Q_0 = 0$


after 2 CLK

$Q_2 = 1, Q_1 = 1, Q_0 = 1$



NOTE: In Parallel in serial out operation preset enable is disabled after obtaining the input data at Q_2, Q_1, Q_0 .

 Ex-1 In following shift register determine the no. of CLK pulses required to bring the shift register to the initial value of 1001. 135




$$\text{Sr. Input} = Q_2 \oplus Q_1 \oplus Q_0$$

CLK	Serial Input $Q_2 \oplus Q_1 \oplus Q_0$	Q_3	Q_2	Q_1	Q_0
0	—	1	0	0	1
1	1	1	1	0	0
2	1	1	1	1	0
3	0	0	1	1	1
4	1	1	0	1	1
5	0	0	1	0	1
6	0	0	0	1	0
7	1	1	0	0	1

So, 7 CLOCK pulse is required.

Ex-2

Initial Value: 0000

 


Clock pulse	A = 0	B = \bar{A}	C = B	D = \bar{C}
—	0	0	0	0
1	0	1	0	1
2	1	1	1	1
3	1	0	1	0
4	0	0	0	0


So, After 4 clock pulse.

* Shift Register Application:

 ① Serial to Parallel / Parallel to serial data Converter.



③ Sequence Generator:

 

④ To generate PN (Pseudo Number) Sequence.


- ⑤ Counter
- (a) Ring Counter
 - (b) Johnson Counter.

NOTE:

→ Shift Register is converted to ring counter by making two changes.

- ① Q_0 is connected to the serial input.
- ② one of the FF is reset.

* 3 - Bit Ring Counter.

 

3:1 Counter \rightarrow Can Count 3 CLK Pulses.

CLK	serial i/p	Q ₂ Q ₁ Q ₀
0	—	1 0 0
1	0	0 1 0
2	0	0 0 1
3	1	1 0 0

\rightarrow Counting:


100 \leftarrow initial value

(a) 001 $\xrightarrow{\text{Decode}}$ 2 clock pulse.

(b) 100 $\xrightarrow{\text{Decode}}$ 3 clock pulse.

(c) 010 $\xrightarrow{\text{Decode}}$ 1 clock pulse.

⇒ Freq division:

 

$$\therefore T_{Q_2} = 3T$$

$$\therefore f_{Q_2} = f/3$$

Similarly,

$$f_{Q_1} = f/3$$

$$f_{Q_0} = f/3$$

⇒ N-bit Ring Counter:

→ N:1 Counter


→ Can count N CLOCK PULSES.

→ Freq. of each FF $Q/p = f/N$.

★ 3-bit Johnson Counter:

(Twisted Counter (or) Switch-tail counter).

 
→ Shift Register can be converted into Johnson Counter by making one change.
i.e. \bar{Q}_0 is connected to the serial i/p.



6:1 Counter.

CLK	serial i/p \bar{Q}_0	Q_2 Q_1 Q_0	Decimal value
0	—	0 0 0	0
1	1 →	1 0 0	4
2	1 →	1 1 0	6
3	1 →	1 1 1	7
4	0 →	0 1 1	3
5	0 →	0 0 1	1
6	0 →	0 0 0	0

⇒ Freq. division:

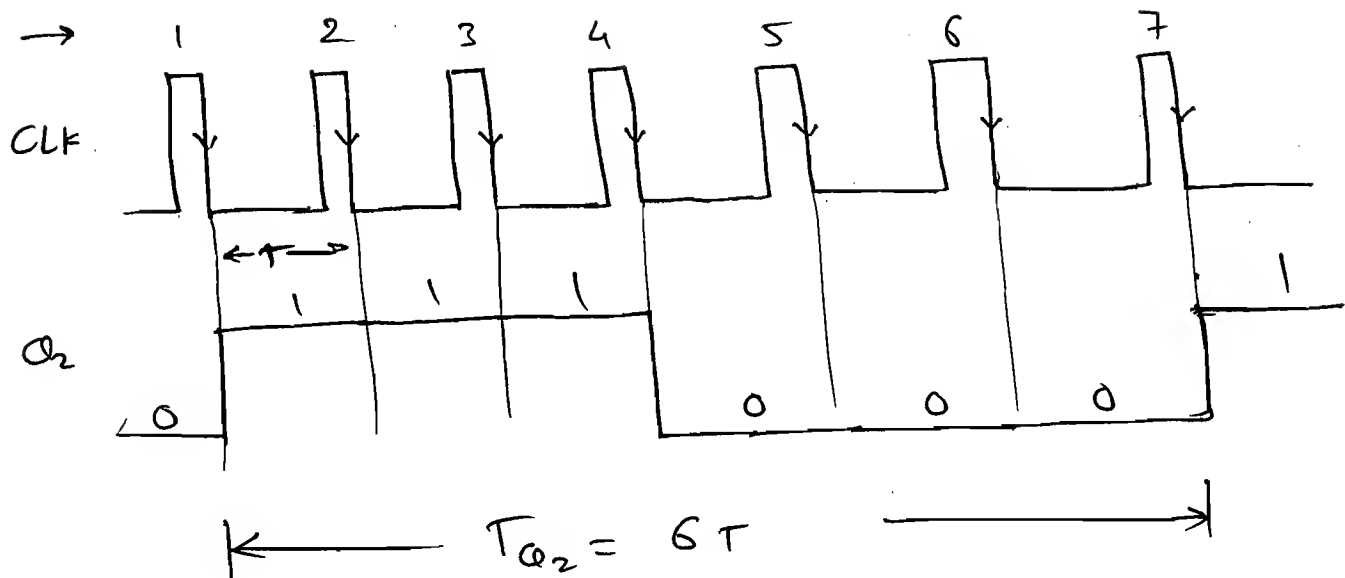

∴ $T_{Q_2} = 6T$

∴ $f_{Q_2} = f/6$

$f_{Q_1} = f_{Q_2} = f/6$

⇒ Counting:

000 ← initial value

a) If 001 → decode → ⑤ CP.

b) If 111 → decode → ③ CP.

c) If 011 → decode → ④ CP.

⇒ N-bit Johnson Counter:

→ $2N+1$ Counter

→ Can count $2N$ CLOCK PULSES.

→ Freq. of each FF o/p = $\frac{f}{2N}$

Ex-1 Determine the o/p freq. of a 3-bit Johnson Counter. If the clock freq. is 18 kHz. Initial value of the counter is 010.

Ans:

CLK	Serial input	Q_2 Q_1 Q_0
0	—	0 1 0
1	1	1 0 1
2	0	0 1 0


\therefore 2:1 counter.

$$\therefore f_o = f/2$$

$$\therefore f_o = \frac{18}{2}$$


$$\therefore \boxed{f_o = 9 \text{ kHz}}$$

 Ex-2 Determine the value of the following ckt after the 729 CP?



→ Given FFs are in toggle mode and are 2 FF.

So,

 

→ The given Counter are a 2 bit Johnson Counter hence the value of counter after 729 CP is same as the value after 1 CP i.e. $Q_1 = 1, Q_0 = 0$

CLK	\bar{Q}_0	Q_1	Q_0
0	-	0	0
1	1	1	0

$$\begin{array}{r}
 182 \\
 4 \overline{) 729} \\
 \underline{4} \\
 32 \\
 \underline{32} \\
 00 \\
 \underline{00} \\
 00 \\
 \underline{00} \\
 00
 \end{array}$$

★ Counter:


① Asynchronous (Ripple) Counter:

→ Any FF, but in toggle mode:

② Synchronous (parallel) Counter:

→ Any FF

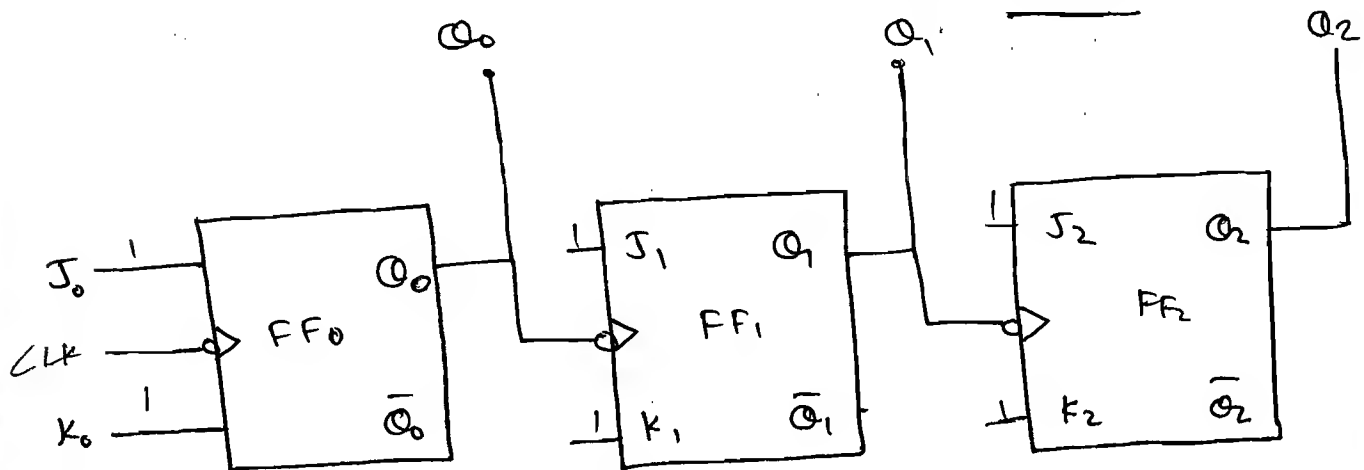① 3-Bit Asynchronous Counter: (UP Counter) (Ripple counter)



→ As $J=K=1 \Rightarrow$ All FFs are in toggle mode.

$$\overline{Q(t+1)} = Q(t).$$

→ Q_0 is toggle for every clock pulse.

→ Q_1 is toggle when Q_0 changes from '1 to 0'

→ Q_2 is toggle when Q_1 changes from '1 to 0'.

CLK	Q ₀ (LSB)	Q ₁	Q ₂ (MSB)	
0	0	0	0	0
1	1	0	0	1
2	0	1	0	2
3	1	1	0	3
4	0	0	1	4
5	1	0	1	5
6	0	1	1	6
7	1	1	1	7
8	0	0	0	8

} Up Counter


$t_{\text{prop}} = 10\text{ns}$

Q₀ is delay by 10ns

Q₁ is delay by 20ns

Q₂ is delay by 30ns

 → freq. is divided by 2 after each flip flop.



* Max. Conv. time = $3 \times 10\text{ns} = 30\text{ns}$.

Clock period $T \geq 30\text{ns}$.

$$\therefore f = \frac{1}{T} \leq \frac{1}{30 \times 10^{-9}}$$



i.e. $f \leq \frac{1}{30 \times 10^{-9}}$

In general,

N-Bit Asynchronous Counter,

$$f \leq \frac{1}{N \cdot t_{pd,PF}}$$

  → Freq. of Async. Counter using strobe pulse.



$$f \leq \frac{1}{N \cdot t_{pd,PF} + T_S}$$


→ Asynchronous Counter uses Strobe
Where as Strobe are not required in
Synchronous.

146

* 3-bit asynchronous Counter. (Down Counter).

→ In the following circuits,

 - (1) Q_0 (toggles) Changes for each clock pulse.
- (2) Q_1 toggles when Q_0 changes from 0 to 1.
- (3) Q_2 toggles when Q_1 changes from 0 to 1.




Note: All FFs are in toggle mode.

CLK	(LSB) Q_0	Q_1	(MSB) Q_2	Decimal
0	0	0	0	0
1	↓	↓	↓	7
2	0 ^x	1	1	6
3	↓	0 ^x	1	5
4	0 ^x	0	1	4
5	↓	↓	0	3
6	0 ^x	1	0	2
7	↓	0	0	1
8	0 ^x	0	0	0

→ Down Counter.

* 2-Bit "Asynchronous Up-Down" Counter.

147

 

→ If $x=0 \Rightarrow \underline{\bar{Q}_0}$ is connected to the clock of next FF.

→ If $x=1 \Rightarrow \underline{Q_0}$ is connected to the clock of next FF.
i.e. 00, 11, 10, 01, 00, ...

→ If $x=1 \Rightarrow \underline{Q_0}$ is connected to the clock of next FF.

\Rightarrow Up Counter
i.e. 00, 01, 10, 11, 00, ...

Imp
NOTE:

In the above Up-Down Counter if the edge triggered FF circuit then

- ① $x=0 \rightarrow$ It act as Up counter.
- ② $x=1 \rightarrow$ It act as Down counter.

Hint (*)

Up Counter


triggering @
 L neg. \rightarrow Positive (or)
 L pos. \rightarrow negative.

(*)


Down Counter

triggering @
 neg. \rightarrow negative
 pos. \rightarrow positive


① Up Counter:

 


(or)

 


② Down Counter:

 

(or)

 

Ex-1

 


Ans

→ FF is -ve edge triggered, $\bar{Q}_0 \rightarrow \text{CLK}$
 hence it is **Down Counter.**

Imp

 
Ex-1 In a 3-bit asynchronous up-Down Counter the clock and control inputs are as given below: Determine the no. of clock pulses required to bring the counter to the initial counting seq. starting with 000.



→ In this Counter each increment requires three clock pulses.

→ To increment 8 times No. of clock pulses are $8 \times 3 = 24$.

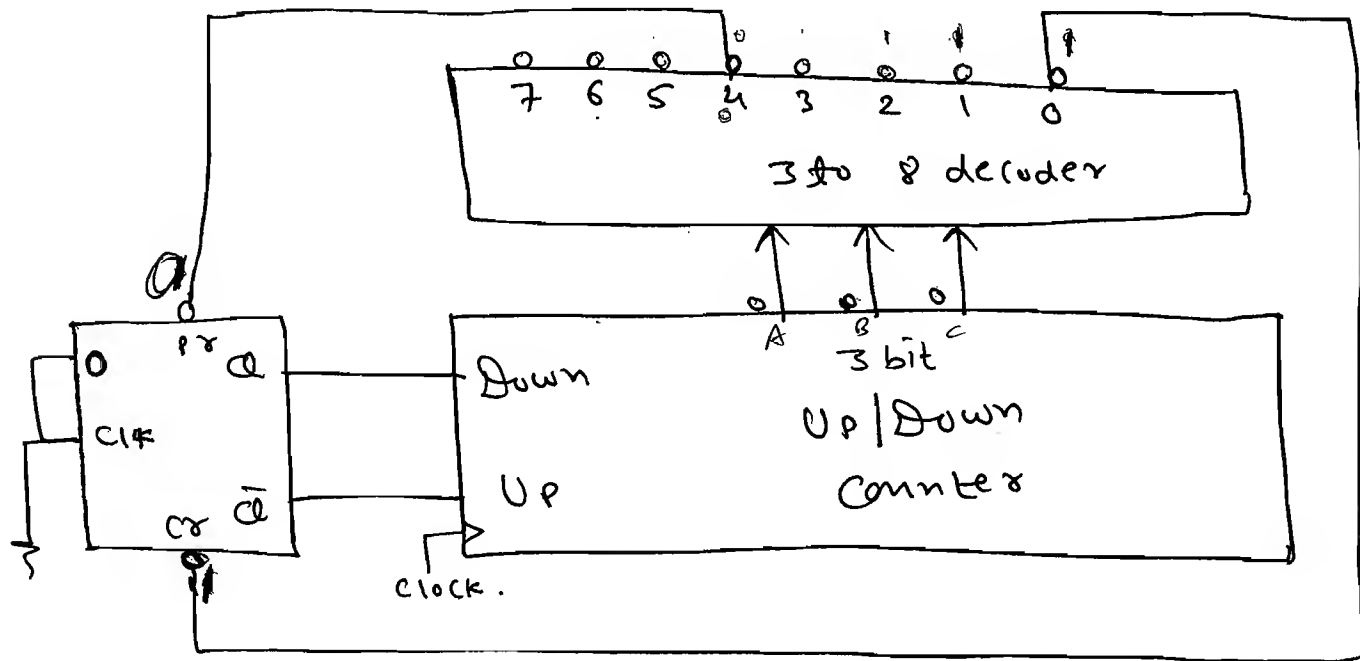Ex-2 In the following Up down Counter determine the counting sequences of the Counter.



Ans:

CLK	A	B	C	
0	0	0	0	
1	0	0	1	UP
2	0	1	0	UP
3	0	1	1	UP
4	1	0	0	UP
5	0	1	1	Down
6	0	1	0	Down
7	0	0	1	Down
8	0	0	0	Down

0, 1, 2, 3, 4, 3, 2, 1, 0, ...

UP DOWN


\therefore $Pr = 1, Cr = 0$ \therefore $Pr = 0, Cr = 1$
 i.e. $Q = 0, \bar{Q} = 1$ i.e. $Q = 1, \bar{Q} = 0$

★ Modulus of a Counter.

→ It is the number of CLK pulses required to bring the counter in the initial state.

→ A Mod-N Counter ^{Counts from 0 to N-1} and output freq. is f/N .

E.g.

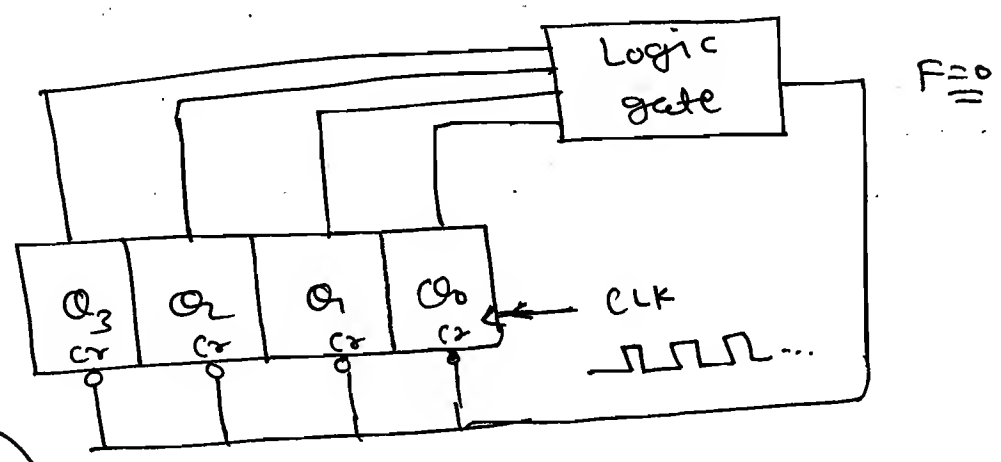


	Q_3	Q_2	Q_1	Q_0
	0	0	0	0
	0	0	0	1
	0	0	1	0
	1	0	0	1
10 →	1	0	1	0
	1	1	1	1

After the required value, F should be zero
 $F=0$.
 i.e for e.g.
 12

* Construct a Mod-6 Asynchronous Counter.

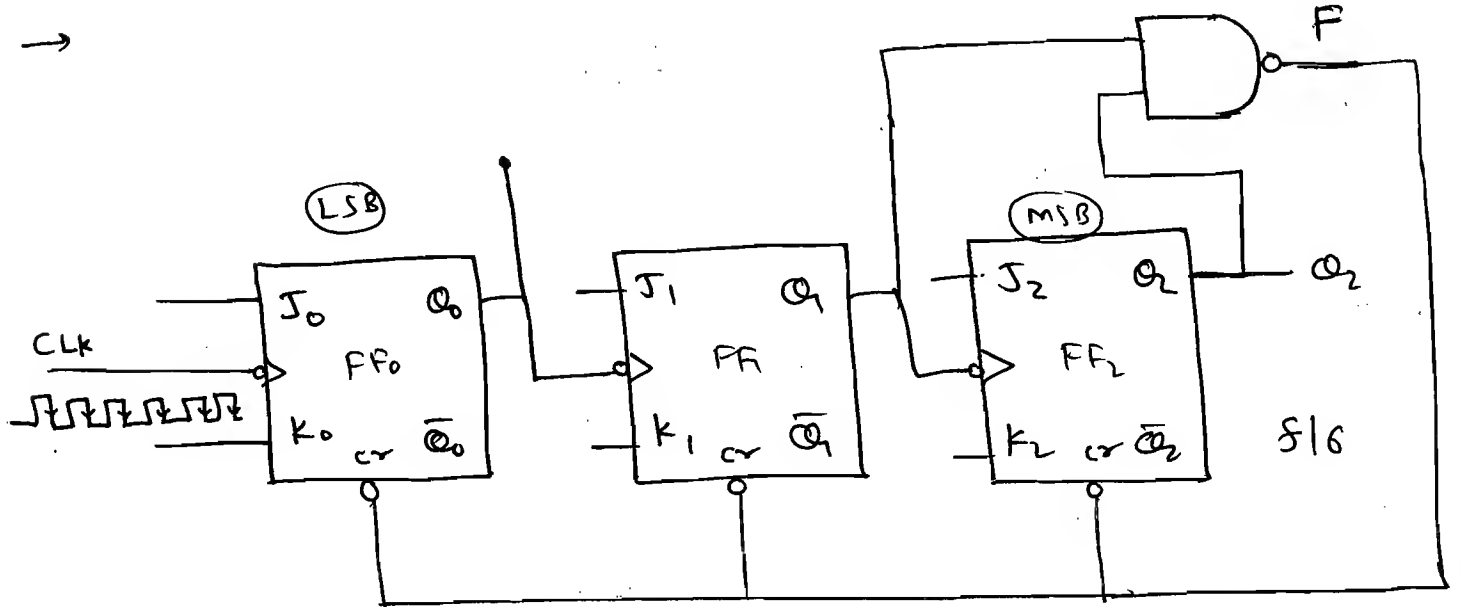→ As soon as it reaches 6 CLK pulse it should be reset.



→ 0 to 5 $\Rightarrow 2^N \geq$ No. of modes of counter.

$$\therefore 2^N \geq 6$$


$$N = 3 \text{ FFs}$$

CLK	Serial inputs	Q_2	Q_1	Q_0	Decimal
0	—	0	0	0	0
1	1	0	0	1	1
2	1	0	1	0	2
3	1	0	1	1	3
4	0	1	0	0	4
5	0	1	0	1	5
6	0	1	1	0	6
		0	0	0	

(i) At 5^{th} CLK pulse $Q_2 = 1, Q_1 = 1$ 139

(ii) Hence when $Q_2 = 1, Q_1 = 1 \Rightarrow$ o/p of gate $F = 0$. All FFs are cleared.


\Rightarrow NAND gate

 

\rightarrow In the above mod-6 asynchronous counter determine the feedback logic gate if its inputs are \bar{Q}_2 & \bar{Q}_1

\rightarrow i.e. $\bar{Q}_2 = 0$ and $\bar{Q}_1 = 0 \Rightarrow$ o/p of gate $F = 0$.


$\therefore \Rightarrow$ OR gate.

 

* Disadvantages:

\rightarrow In Asynchronous counters whose modulus is not equal to 2^N the output produces unwanted spikes called as glitches.

Eg.

 


→ Latch output is latched on input; output doesn't change even if input changes



- ② If the FF are having unequal clearing times then all the FF cannot be cleared at the required clock pulse. To overcome this a latch is used in the feedback path such that its output remains zero until all the FF are cleared.

 
Ex-1 Determine the modulus of the following Asynchronous Counter:



→ For $Q_3 Q_2 Q_1 Q_0 = 1000$ → All the FFs are cleared.

→ It is Mod-10 Counter (decade counter)

(b)

 

Ans:

\odot_3 \odot_2 \odot_1 \odot_0
 \circ \circ \circ \circ
 \circ \circ \circ $|$
 ?

$$f \propto \frac{1}{2}$$

4 will appear
first
i.e. 01. will
appear first than
10.

0 1 2 3 ~~4~~

For $Q_3 Q_2 Q_1 Q_0 = 0100 \rightarrow$ All the FFs are cleared.
 \rightarrow It is Mod - 4 Counter.

→ The disadvantages of Asynchronous Counter is the freq. of operation is inversely proportional to the no. of FFs. To overcome this we use Synchronous or Parallel Counters.

* Flip Flop Excitation table:

① S-R FF:

$Q(t)$	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

② D-Flip Flop:

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

③ T-Flip Flop:

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

④ J-K-Flip Flop:

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$Q(t)$	$Q(t+1)$	FF Inputs					
		J	K	S	R	D	T
0	0	0	X	0	X	0	0
0	1	1	X	1	0	1	1
1	0	X	1	0	1	0	1
1	1	X	0	X	0	1	0

Ex-1 Determine the excitation table of X-Y FF whose T.T. is as given below.

X	Y	$Q(t+1)$
0	0	1
0	1	$Q(t)$
1	0	$\overline{Q(t)}$
1	1	0


$Q(t)$	$Q(t+1)$	X	Y
0	0	X	1
0	1	X	0
1	0	1	X
1	1	0	X

* Design a Synchronous Counter using J-K Flip Flops. which comes through the states 0, 1, 2, 4, 5, 6, 0, ...

(b) is it a self starting Counter?

Ans:

(a) State Diagram.

 

(b) State Assignment:

① → 000

② → 001

③ → 010

④ → 100

⑤ → 101

⑥ → 110.

(c) Excitation Table:

	FF Inputs			$J_2 K_2$	$J_1 K_1$	$J_0 K_0$
	Q_2	Q_1	Q_0			
⑥	0	0	0	0 X	0 X	1 X
①	0	0	1	0 X	1 X	X 1
②	0	1	0	1 X	X 1	0 X
④	1	0	0	X 0	0 X	1 X
⑤	1	0	1	X 0	0 X	1 X
⑥	1	1	0	X 1	X 1	0 X
⑦	0	0	0			

* ③, ⑦ are unused states. Takes them as don't cares.

$$J_0 = \bar{Q}_1 \quad K_0 = 1$$

$$J_1 = Q_1 + Q_2 \quad K_1 = 1$$

$$J_2 = Q_1 \quad K_2 = Q_1$$

$Q_1 Q_2$	00	01	11	10
Q_0				
0	0	0	X	1
1	X	X	X	X

$$J_2 = Q_1$$

$Q_1 Q_2$	00	01	11	10
Q_0				
0	X	X	X	X
1			X	1

$$K_2 = Q_1$$


$Q_1 Q_2$	00	01	11	10
Q_0				
0	X	X	X	
1	1	X	X	

$$J_0 = \bar{Q}_1$$

$Q_1 Q_2$	00	01	11	10
Q_0				
0		X	X	X
1		1	X	X

$$J_1 = Q_2 + Q_1$$

Ex/2 Sum

 


→ In Sync Counter, Freq of operation

$$f \leq \frac{1}{t_{pd} \cdot FF}$$

(b)

	Present State			FF Inputs			Next State		
	Q_2	Q_1	Q_0	J_2, K_2	J_1, K_1	J_0, K_0	Q_2	Q_1	Q_0
③ →	0	1	1	<u>1</u> <u>1</u>	<u>1</u> <u>1</u>	<u>0</u> <u>1</u>	1	0	0
⑦ →	1	1	1	<u>1</u> <u>1</u>	<u>1</u> <u>1</u>	<u>0</u> <u>1</u>	0	0	0

 

It is a self starting counter as we get ③ after ② and ① after ⑦.

→ The above Counter is a self starting Counter because it is able to enter the used states from all unused state.

e.g. of non self starting Counter




Ex-2

A Synchronous Counter comes through the states 0, 3, 5, 6, 0, ... and FF inputs are $T_2 = Q_1$, $T_1 = 1$, $T_0 = \bar{Q}_1$. Is it a self starting Counter.


⇒ Table for analysis:

	Pr. State			FF Inputs			Next State		
	Q_2	Q_1	Q_0	$T_2 = Q_1$	$T_1 = 1$	$T_0 = \bar{Q}_1$	Q_2	Q_1	Q_0
①	0	0	1	0	1	1	0	1	0
②	0	1	0	1	1	0	1	0	0
④	1	0	0	0	1	1	1	1	1
⑦	1	1	1	1	1	0	0	0	1

Used state

 

Unused state

 


'Lock-out' of Counter

→ It is an ~~in~~ ^{an} ~~ebicet~~ ^{asynchronous} counter.

Not a self starting Counter.


→ To avoid the Lock-out condition

 ① Redesign the Counter according to the following state diagram.



→ No. of PF state is increasing \Rightarrow no. of PF is increased in it will increase the complexity of ckt

 ② Clearing the Counter as soon it enters into Unused state. as shown below:



$$F(Q_2, Q_1, Q_0) = \sum m(1, 2, 4, 7).$$

	Q_2	Q_1	Q_0
Q_2			

$$\therefore F = Q_2 \oplus Q_1 \oplus Q_0$$

(OR)

$$F = Q_2 \odot Q_1 \odot Q_0$$

NOTE:

⇒ In the above synchronous counter the Combinational Logic is determined as follows:

→ When Counter enters into the states ①, ②, ④, ⑦ the F should become 1. So, then the Counter can be clear.

→ The sum of minterm expression for F is

$$F(Q_2, Q_1, Q_0) = \Sigma(1, 2, 4, 7).$$


	Q_2	Q_1	Q_0
Q_2			

$$\therefore F = Q_2 \oplus Q_1 \oplus Q_0$$

(OR)

$$F = Q_2 \odot Q_1 \odot Q_0$$

 Ex-2 Determine the modulus of the following counter




Ans: 'Q' is in Asynchronous mode. It toggles when Q_0 changes from 1 to 0.

now $J_0 = \bar{Q}_2$, $J_2 = Q_0 Q_1$
 $K_0 = 1$, $K_2 = 1$.

⇒ Table for analysis:

P.S.	FF Inputs		N.S.		
	Q_2	Q_1	Q_0	$J_2 K_2$	$J_0 K_0$
⑤	0	0	0	0 1	1 1
①	0	0	1	0 1	1 1
②	0	1	0	0 1	1 1
③	0	1	1	1 1	1 1
④	1	0	0	0 1	0 1

 

"Modulus = 5".

158
 \rightarrow If $t_{pd,FF} = 10\text{ns}$ \rightarrow $t_{max} = ?$

Max. Conv. time = $10 + 10 = 20\text{ns}$.


C :: FF₀, FF₂ are in synch. mode,
 FF₁ is in Async mode].

Clock period $T \geq 20\text{ns}$.

$$\therefore f \leq \frac{1}{20 \times 10^{-9}}$$

$$\therefore f_{max} = \frac{1}{20 \times 10^{-9}} \text{ Hz}$$

 Ex-3 Determine the fn of the following
 seq. circuits by obtaining its state
 diagram.




	P.S.		FF inputs		N.S.	
	A	B	TA	TB	A	B
①	0	0	0	1	0	1
①	0	1	1	1	1	0
②	1	0	1	0	0	0
③	1	1	1	1	0	0

$$T_A = A + B$$

$$T_B = \bar{A} + B$$

State diagram

 

→ it is a Mod-3, self starting synchronous counter.


* State Diagram:

Hint:

 
- (i) No of states = 2^N ; N = No of FFs
- (ii) No of branches from each state = 2^x ;
 x = no of direct inputs.

① 2-Bit Up/Down Sync Counter:

→ 2 FFs \Rightarrow No. of states = $2^2 = 4$.



 
→ 1 direct inp (i.e. x) \Rightarrow No. of branches from each state = $2^1 = 2$.



[State Diagram]


② J-K FF state diagram:

 - 1 FF \Rightarrow 2 states ($Q=0, Q=1$).
- 2 Direct input \Rightarrow 4 branches from each state.



Q(k)	J	K	Q(k+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

③ Gate - 2013

 

→ 1 FF \Rightarrow 2 States ($Q=0, Q=1$).

→ Input (i.e. A) \Rightarrow 2 branches from each state.

For D-FF $\rightarrow Q(t+1) = D$ — ①


For MUX $\rightarrow D = \bar{A} \cdot \bar{Q} + A \cdot Q$ — ②

from ① & ②

$$\therefore Q(t+1) = \bar{A} \cdot \bar{Q}(t) + A \cdot Q(t).$$


When $A=0$, $Q(t+1) = \bar{Q}(t)$

$A=1$, $Q(t+1) = Q(t)$

 

④ Serial Adder State diagram:


183
160

 


→ 2/inputs 1 FF → 2 states ($z=0, z=1$).

→ 2 input → $2^2 = 4$ branches from each state.

P.S. (z)	input x y		N.S. C_{i+1}	output Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1

 


Ex-1 Identify the following FFs.

 

x	$Q(t+1)$
0	0
1	1

→ T-FF State diagram

 

x	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

Input = $\boxed{1 \ 0 \ 1 \ 0}$


output = $\boxed{0 \ 1 \ 1 \ 0}$

→ It is 2's comp. of binary no.

→ so, $\boxed{\text{it is 2's complement circuit}}$

* Conversion of Flipflops:

⇒ Universal Principle:

 

Ex-1 Convert S-R FF to T flip flop.

167
162

Ans: Step-① → Characteristics table of T-Flip flop.
Step-② → Excitation table of SR flip flop.

T	Q(t)	Q(t+1)	S	R
0	0	0	0	x
	1	1	x	0
1	0	1	1	0
	1	0	0	1


→ ③

T	Q(t)	
	0	1
0	0	x
1	①	0

$$S = T\bar{Q}(t).$$


T	Q(t)	
	0	1
0	x	0
1	0	①

$$R = TQ(t).$$

 

[T-Flip Flop]

 Ex-2 In the following diagram determine the
Combinational logic to be used.



Given

X	Y	Q(t+1)	S	R
0	0	0		
0	1	Q(t)		
1	0	$\bar{Q}(t)$		
1	1	1		

X	Y	Q(t)	Q(t+1)	S	R
0	0	0	0	0	X
0	0	1	0	X 0	0 1
0	1	0	0	0	X
0	1	1	1	X	0
1	0	0	1	1	0
1	0	1	0	0	1
1	1	0	1	1	0
1	1	1	1	X	0

① S


	$y a(t)$			
	00	01	11	10
X	0	0	X	0
0	0	0	X	0
1	1	0	X	1

$\therefore S = \cancel{X} \cancel{0} X \bar{0}(t)$


② R

	$y a(t)$			
	00	01	11	10
X	0	0	0	0
0	X	0	0	0
1	0	1	0	0

 $\therefore R = \cancel{X} \bar{1} 0(t)$
 $R = \bar{y} 0(t)$



 Ex-3 (a) Identify the following flip flop.



$T = x \oplus a(t) \quad \text{--- (1)}$


For T FF
 $T \Rightarrow a(t+1) = T \oplus a(t)$

$a(t+1) = x \oplus a(t) \oplus a(t)$

$\therefore a(t+1) = x \oplus 0$
 $\boxed{a(t+1) = x}$

We know \Rightarrow ③ is similar to D-FF Character
 \Rightarrow It is D-Flip Flop.

b)

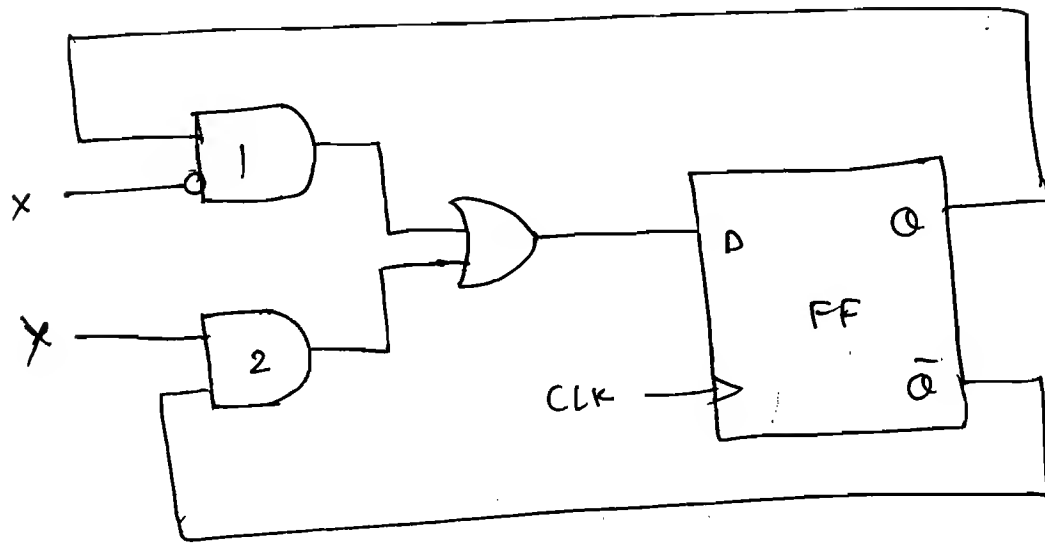

$$D = Q\bar{X} + \bar{Q}Y.$$

$$\therefore Q(t+1) = Q(t)(\bar{X}) + \bar{Q}(t)(Y). \quad \text{--- ③}$$

$$\begin{matrix} J\bar{Q} & \bar{J}Q \\ K\bar{Q} & KQ \end{matrix}$$

$$\therefore Q(t+1) = (\bar{J})\bar{Q}(t) + (K)Q(t). \quad \text{--- ④}$$

$$\text{So, } \bar{X} = \bar{J}$$

$$\boxed{X = J}$$


$$\boxed{X = K}$$

$$\boxed{Y = J}$$

$$\boxed{\begin{matrix} X = K \\ Y = J \end{matrix}}$$

So, it is J-K flip flop.

Full Subtractor using NOR gate only.

 

$$D = A \oplus B \oplus b_i$$

$$B = b_i(A \odot B) + \bar{A}B$$

$$A \oplus B + [b_i + A \odot B]$$

$$= \overline{A \odot B} [b_i + A \odot B]$$


$$= (A \odot B) b_i$$

$$= A \oplus B \oplus b_i$$

$$B = b_i(A \odot B) + \bar{A}B$$

* Full Subtractor using NAND gate only:

 
$$\overline{A \oplus B} = \overline{A} + B = \overline{A}B$$



$$D = A \oplus B \oplus b_i$$

$$B = b_i(A \oplus B) + \overline{A}B$$

* Full Adder using NOR gate only:

 


$$S = A \oplus B \oplus C_i$$

$$C_{i+1} = C_i (A \oplus B) + AB$$

$$C_{i+1} = C_i (A \oplus B) + AB$$

* Full Adder using NAND gate only

 

$$S = A \oplus B \oplus c_i$$

$$c = c_i(A \oplus B) + AB$$

$$c_{i+1} = \overline{AB \cdot c_i(A \oplus B)}$$

$$= AB + c_i(A \oplus B)$$

